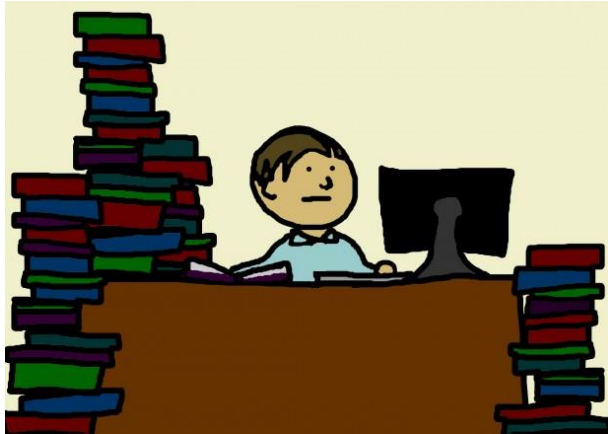


# **FSM 2 : Finite State Machines**

---

# Let's Try This Out...

---




Bob is stressed out as he has too many deadlines and isn't sleeping enough! He has decided to develop a FSM to regulate his time between sleeping and studying.


- When he is idle, there are two actions he can do next : SLEEP or STUDY.
- To prevent exhaustion, he buys a body exhaustion sensor and checks it every hour. When he is exhausted, the sensor output EX will be TRUE.
- When he is exhausted, he should sleep (SLEEP is TRUE). When he is not exhausted, he should study (STUDY is TRUE).
- Implement his FSM using D Flip Flops and gates.

# Step 1 : Block Diagram, STD

1) Block Diagram

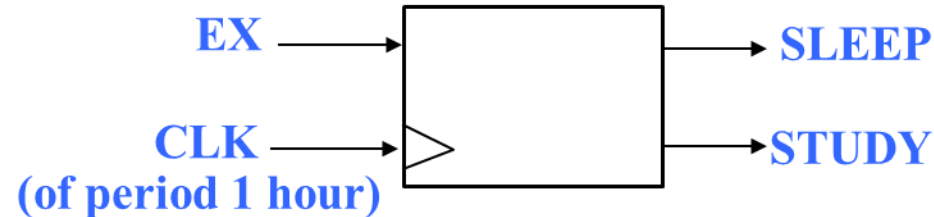


2) State Transition Diagram

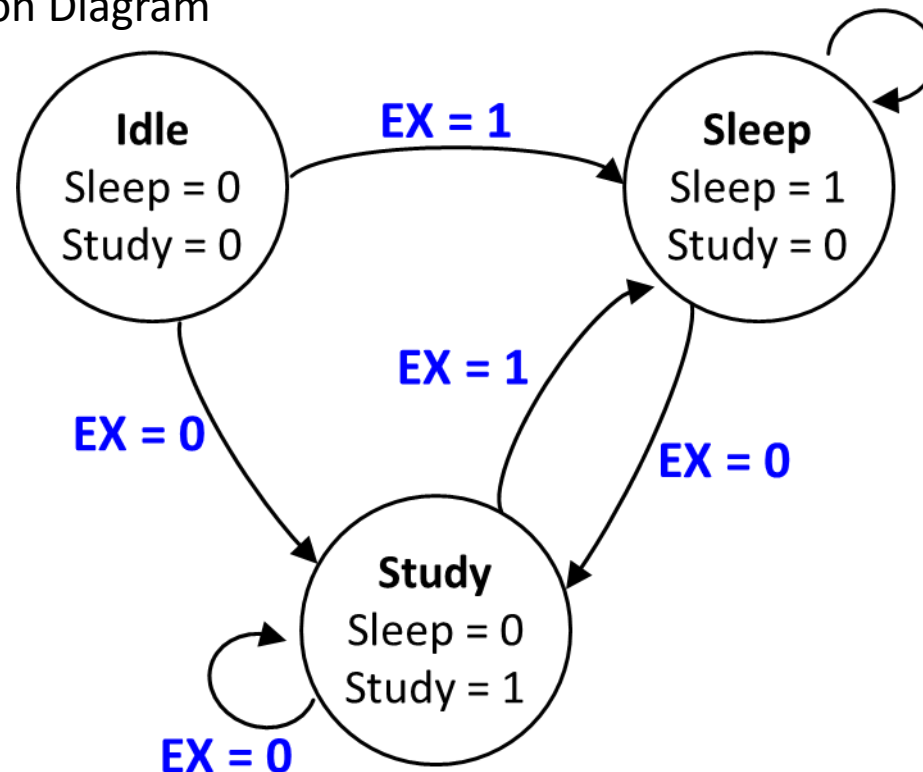

# Step 2 : Next State Table

State Transition Diagram

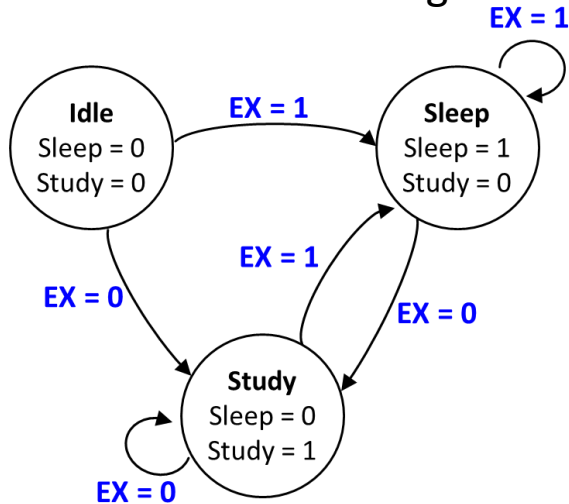

| $S_1S_0$ | EX | $S_1+S_0+$ |
|----------|----|------------|
| 0 0      | 0  | 1 0        |
| 0 0      | 1  | 0 1        |
| 0 1      | 0  | 1 0        |
| 0 1      | 1  | 0 1        |
| 1 0      | 0  | 1 0        |
| 1 0      | 1  | 0 1        |

Current State Input Next State

| S     | EX | S+    |
|-------|----|-------|
| IDLE  | 0  | STUDY |
| IDLE  | 1  | SLEEP |
| SLEEP | 0  | STUDY |
| SLEEP | 1  | SLEEP |
| STUDY | 0  | STUDY |
| STUDY | 1  | SLEEP |

| State | $S_1S_0$ |
|-------|----------|
| IDLE  | 00       |
| SLEEP | 01       |
| STUDY | 10       |

# Step 2 : Next State Table

| $S_1S_0$ | EX | $S_1+S_0+$ |
|----------|----|------------|
| 0 0      | 0  | 1 0        |
| 0 0      | 1  | 0 1        |
| 0 1      | 0  | 1 0        |
| 0 1      | 1  | 0 1        |
| 1 0      | 0  | 1 0        |
| 1 0      | 1  | 0 1        |

| $D_1 =$ |
|---------|
| 1       |
| 0       |
| 1       |
| 0       |
| 1       |
| 0       |

| $D_0 =$ |
|---------|
| 0       |
| 1       |
| 0       |
| 1       |
| 0       |
| 1       |

$D_1$ :

| $S_1S_0$ | 00 | 01 | 11 | 10 |
|----------|----|----|----|----|
| EX       |    |    |    |    |
| 0        | 1  | 1  | X  | 1  |
| 1        | 0  | 0  | X  | 0  |

$$S_1+ = \overline{EX}$$

$D_0$ :


| $S_1S_0$ | 00 | 01 | 11 | 10 |
|----------|----|----|----|----|
| EX       |    |    |    |    |
| 0        | 0  | 0  | X  | 0  |
| 1        | 1  | 1  | X  | 1  |

$$S_0+ = EX$$
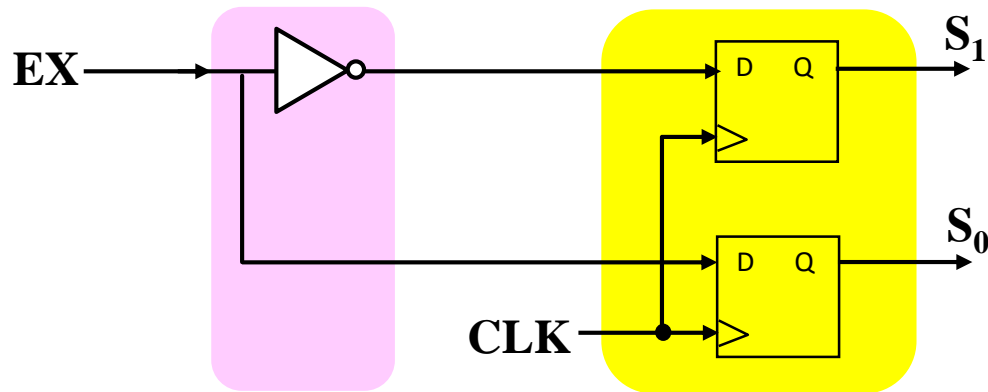
# Step 2 : Next State Table


---

If the state assignments were to change, would the next state logic change?



# Step 3 : Output Logic


| State | $S_1S_0$ |
|-------|----------|
| IDLE  | 00       |
| SLEEP | 01       |
| STUDY | 10       |

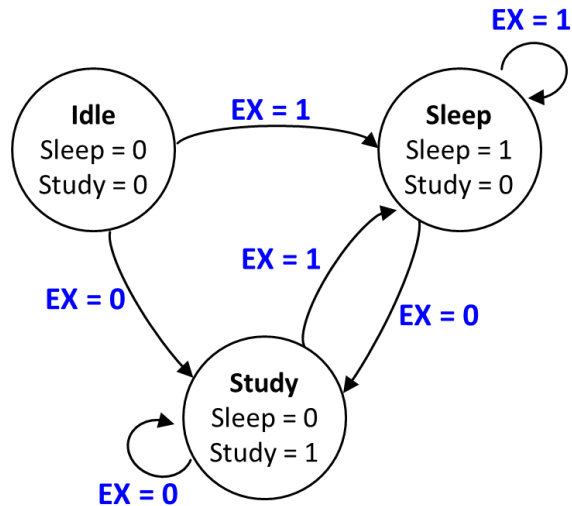

| $S_1S_0$ | Sleep | Study |
|----------|-------|-------|
| 0 0      | 0     | 0     |
| 0 1      | 1     | 0     |
| 1 0      | 0     | 1     |

$$\text{Sleep} = \overline{S_1}S_0$$

$$\text{Study} = S_1\overline{S_0}$$

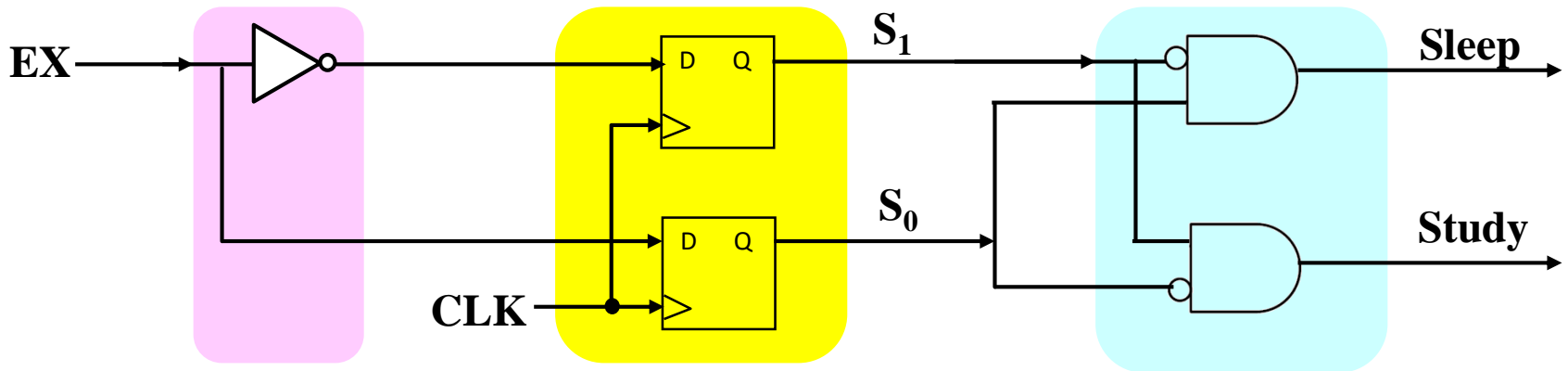


# Changing Sleep Time...



Bob has decided that he is sleep state for too long and has decided to fix his sleep time to 5 hours.

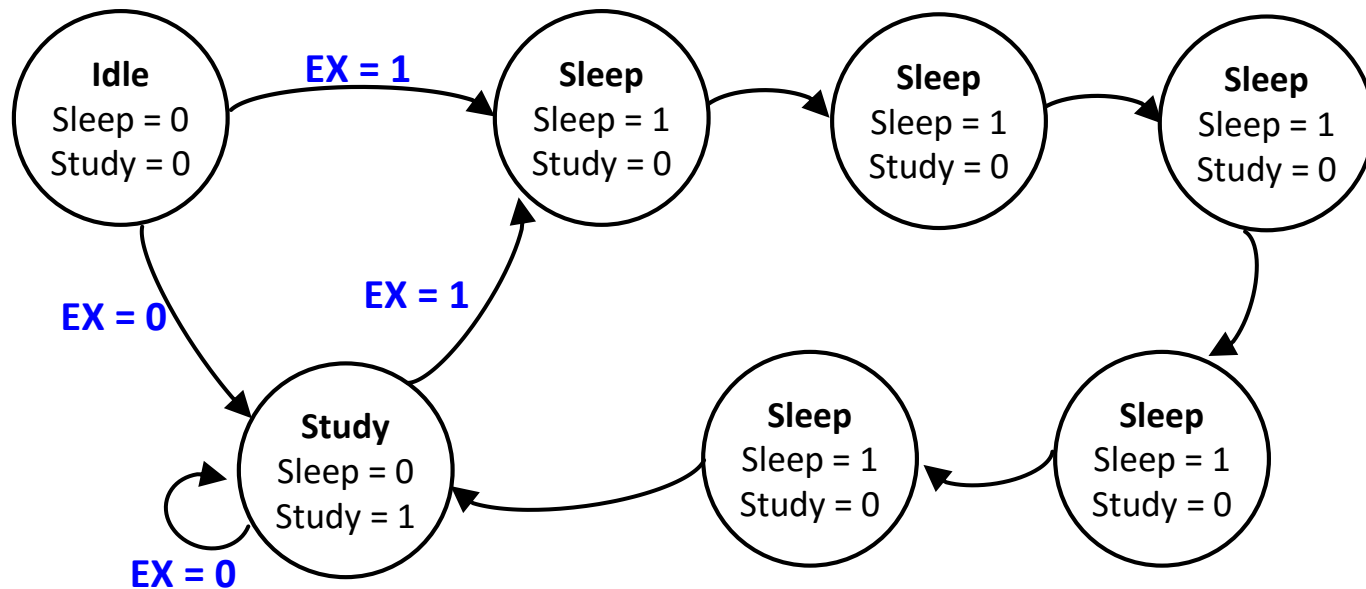
## How can we modify his state transition diagram?





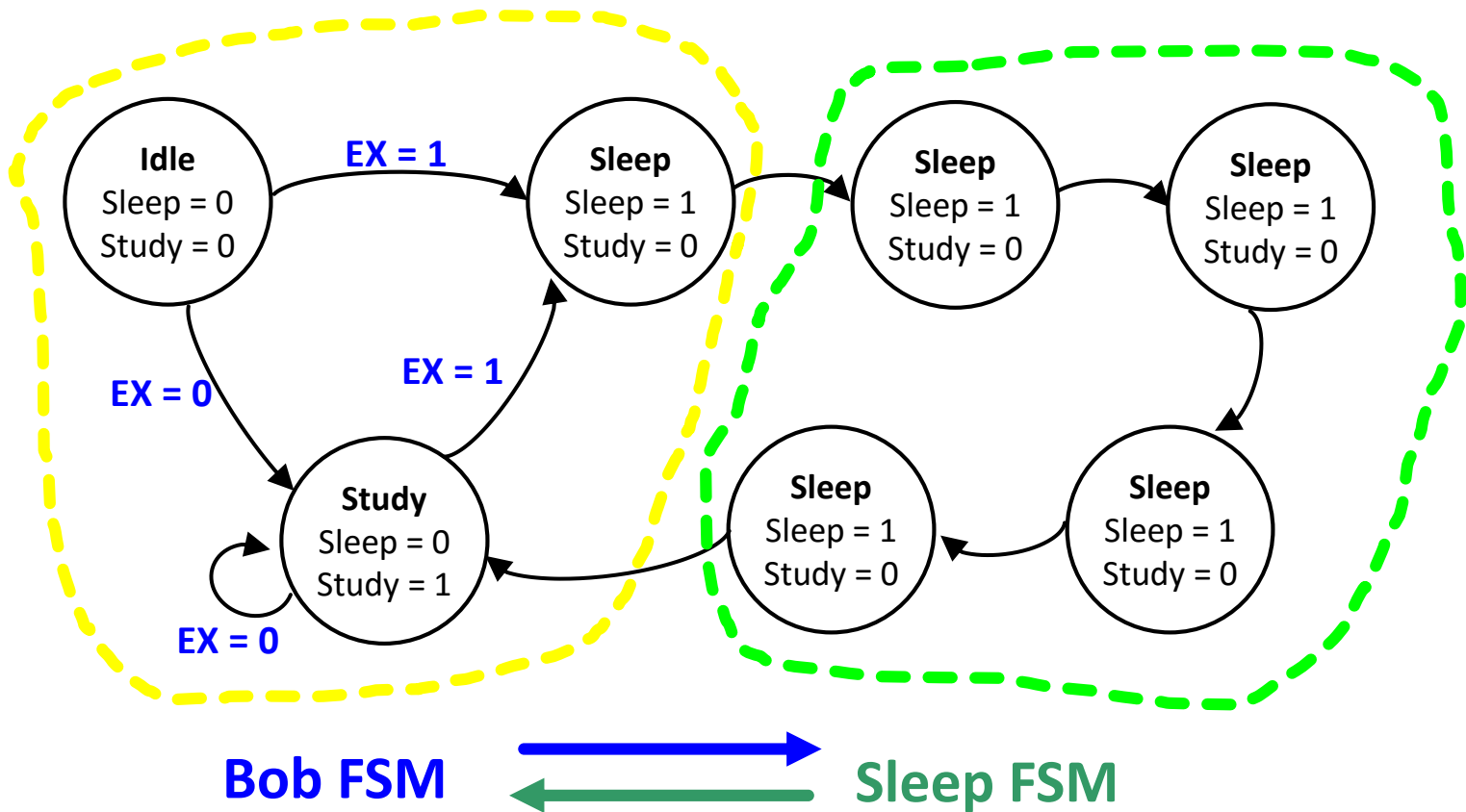
# Modular Design of FSMs

Designing complex FSMs is often easier if they can be broken down into simpler FSMs that interact.




# Modular Design of State Machines

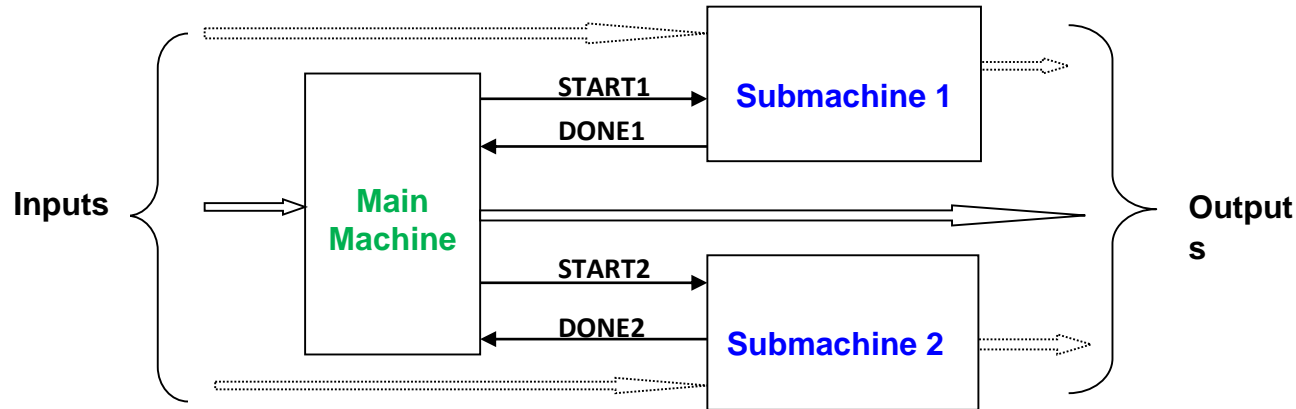

- **Main machine** : executes main algorithm, controls the **submachines** & get the job done. Commands & gets feedback signals from **submachines**.
- **Submachines** respond to external inputs & commands from **main machine**. Can give outputs as well as feedback to the **main machine**.
- Common examples of **submachines** are **counters**, **shift registers**, etc.
- Sometimes the **main machine** is called the **controller** and the **submachines** are called **controlled circuit elements** or **architectural elements**.
- **Trick here** is to **modularize** appropriately, and pick suitable components for the submachines that simplify the design problem.

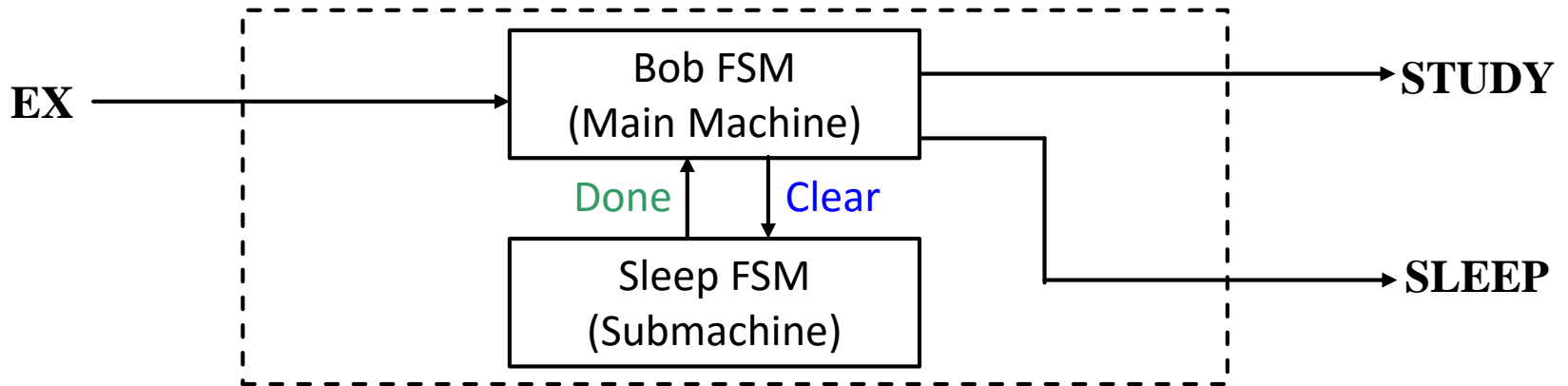
# Modularizing...

What is a natural submachine that we can use?




What inputs would you provide? What outputs would you want?

Mod-5 Counter

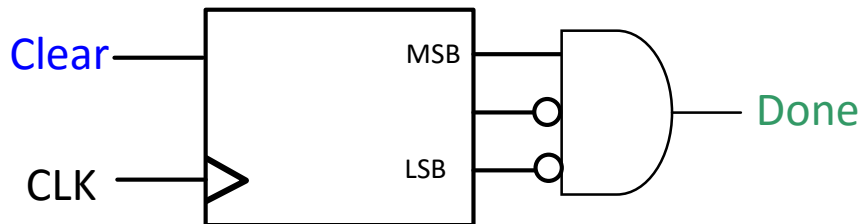


**Done = 1** when count = 4

Mod-X Counter

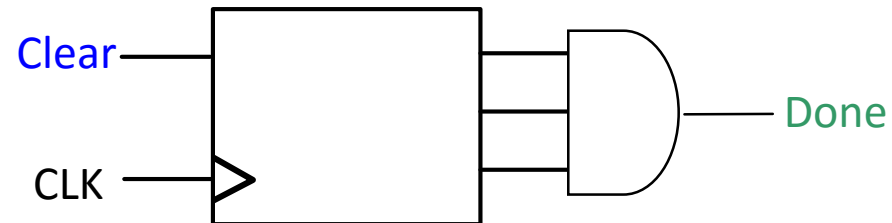


**Done = 1** when count = (X-1)

# Modified FSM

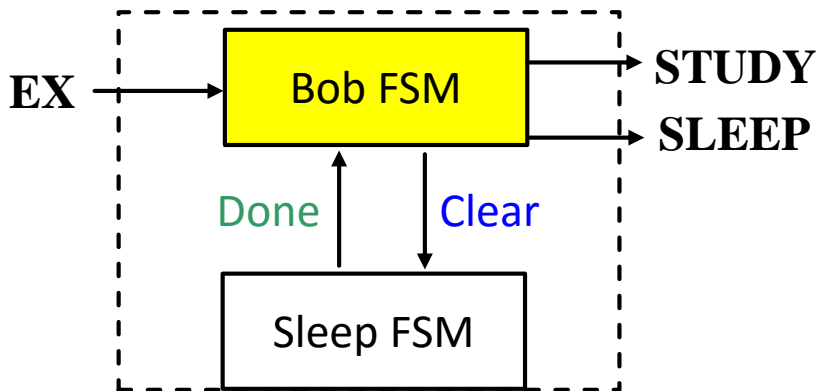


## Sleep FSM



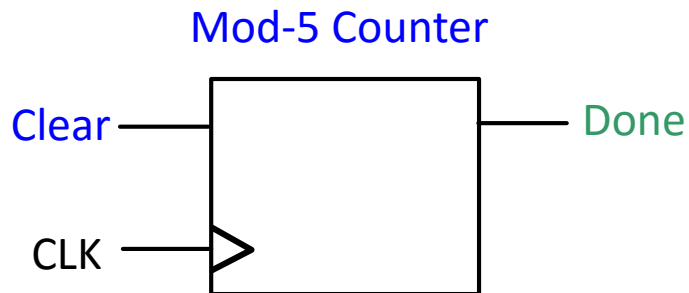




**Done = 1** when count = 4 (100)

## Bob FSM

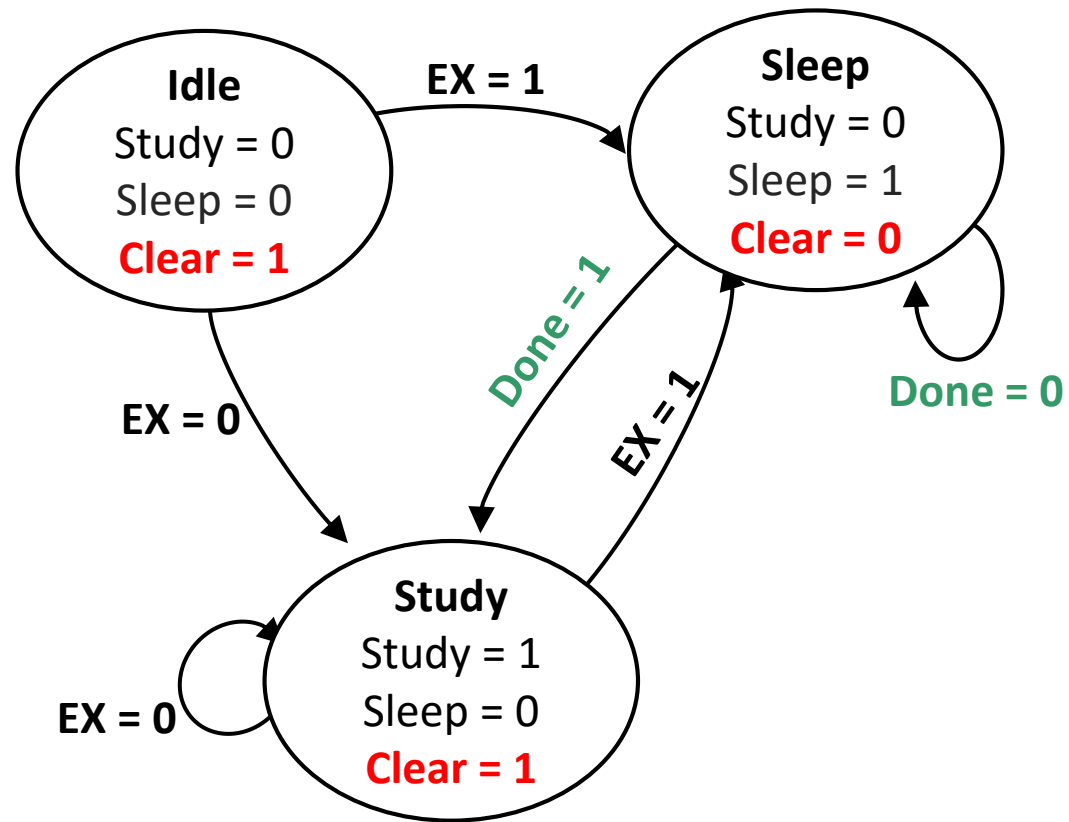


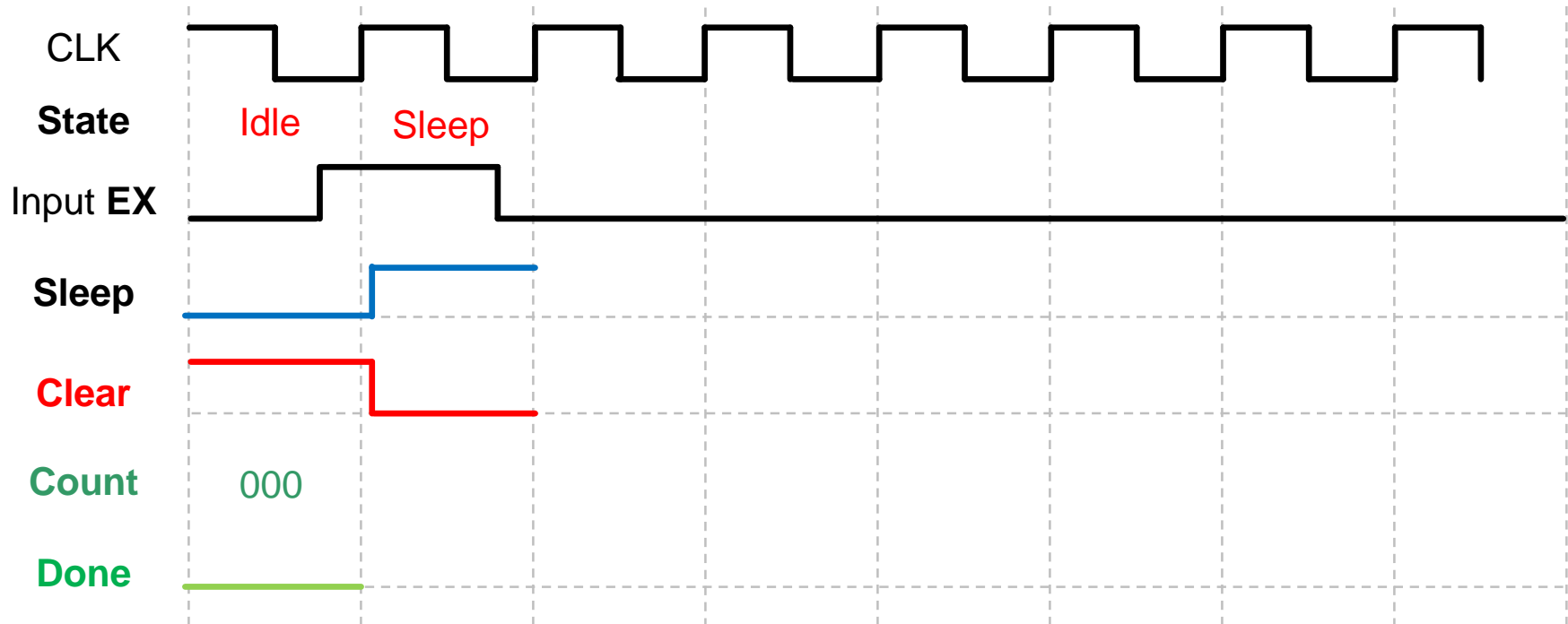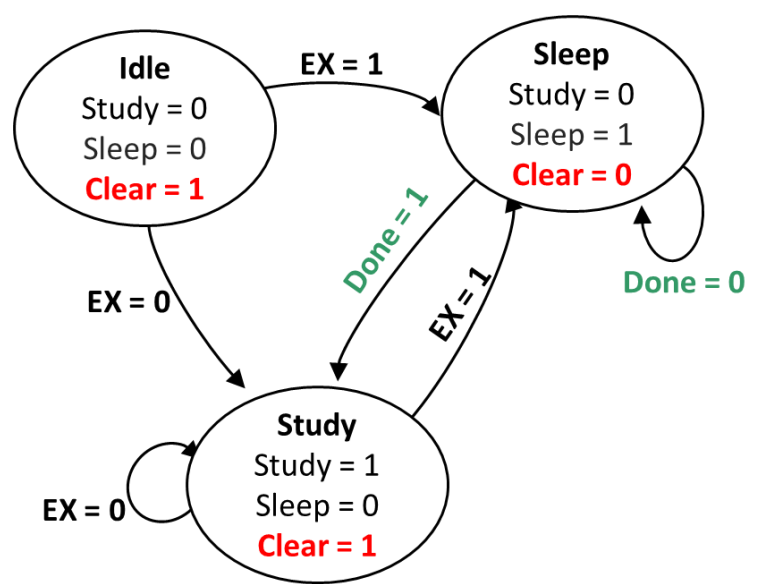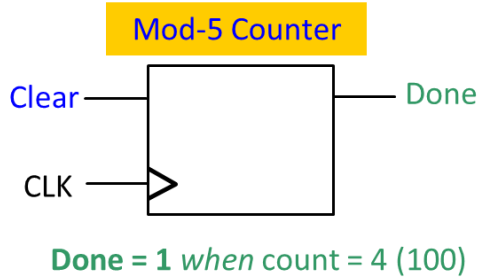Fill in the timing diagram for Bob  
FSM and the counter.



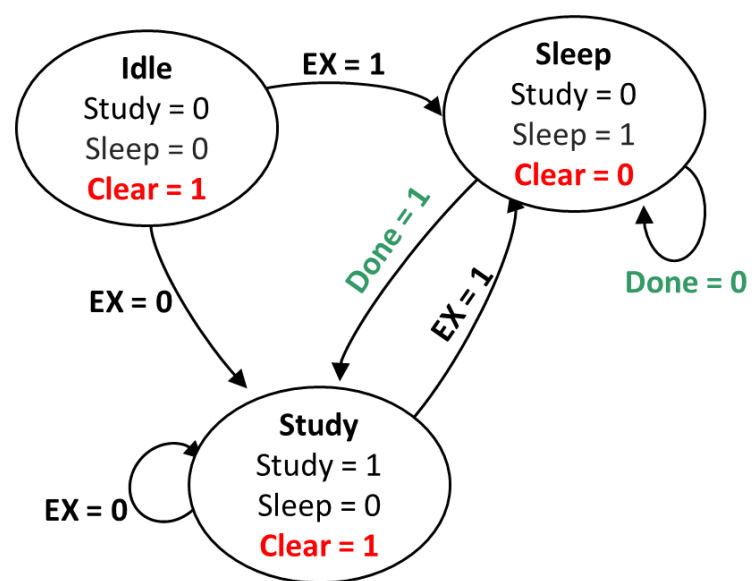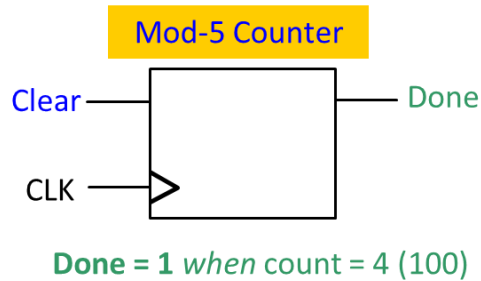

## Timing Diagram:

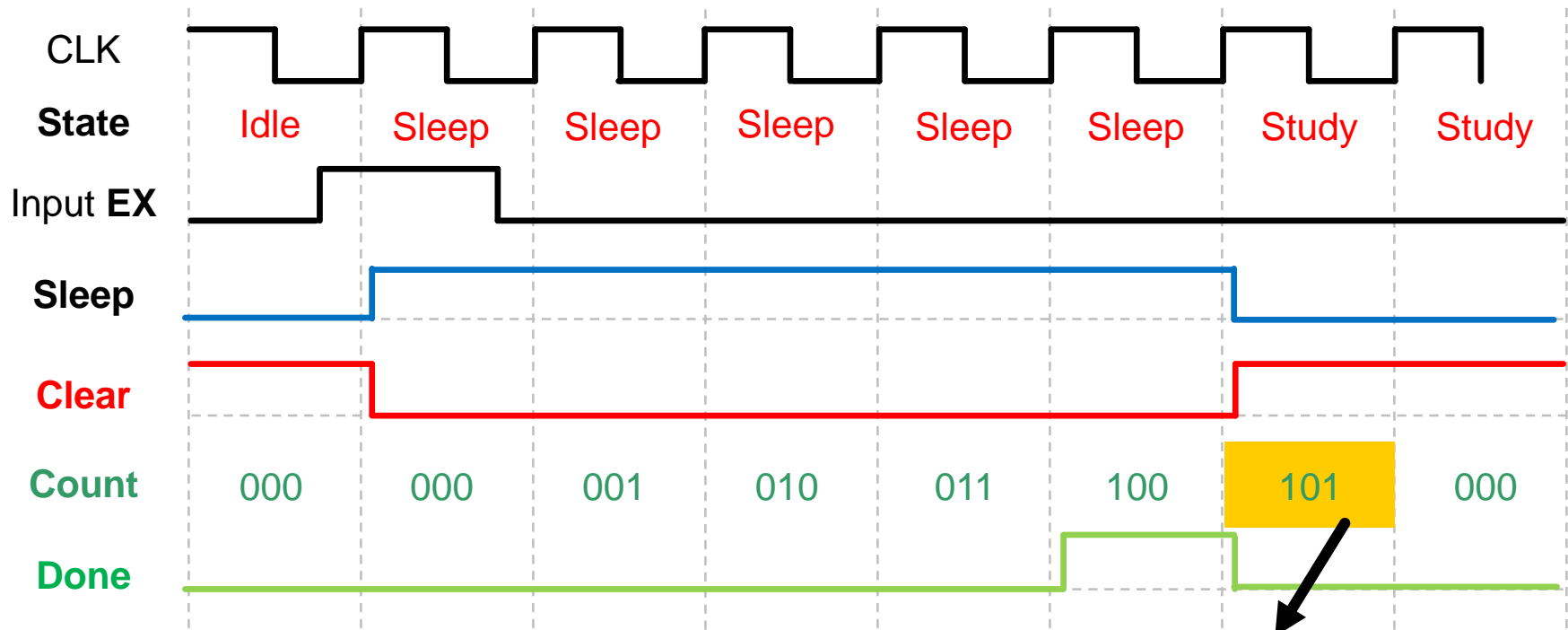

For a mod-5 counter, this should be 000. However, notice that even if the count continues to increase, operation of Bob FSM is not affected! Page 15