 



Tutorial 6 Questions

Flip Flops



- Q1. The D and CLK/ENABLE input waveforms shown below are applied to a negative-edge triggered D flip-flop & a D Latch. Clearly draw the output Q waveforms of the devices and neglect all propagation delays.



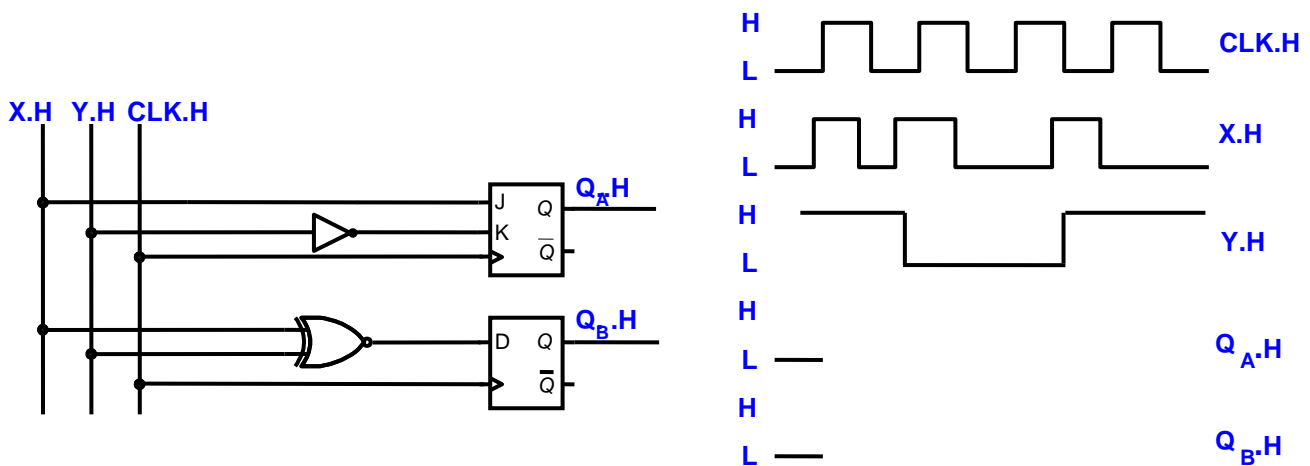- Q2. Given the circuit diagram below, complete the timing diagram below by filling in Q_A and Q_B . Include the propagation delays t_{PHL} and t_{PLH} .



  - Q3. (a) Given the circuit diagram below, complete the timing diagram below by filling in J, K and Q. Neglect all propagation delays in this question.
- (b) If the circuit below represents a type of AB flip flop, fill in its characteristic table and condensed characteristic table below.



A	B	Q	Q ⁺

Characteristic Table

A	B	Q ⁺

Condensed Characteristic Table