

VERILOG for Sequential Circuits




©COPYRIGHT CHUA DINGJUAN. ALL RIGHTS RESERVED.


What are HDLs?

Hardware Description Languages (HDLs) are programming languages for describing digital circuits and systems.

CONCURRENCY

 

STRUCTURE & TIME

 

Today, **Verilog** and **VHDL** are the two leading HDLs.

Combines dataflow, structural and behavioral modeling styles.

Virtually every chip (FPGA, ASIC, etc.) is designed in part using one of these two languages.

Xilinx and Altera are the two largest FPGA manufacturers.

Verilog...

Verilog is an IEEE 1364 Standard → link [here](#)

Used for ***Modeling, Simulation*** and ***Synthesis*** of digital circuits.

Advantages :


- Reduces Design Time → Cost
- Improves Design Quality
- Vendor and Technology Independence
- Easy Design Management

Disadvantages :

- Cost (Including training you and me!)
- Debugging

The Module

 A piece of hardware with inputs & outputs : *module*




Module Name	Port Declaration
<code>module bigbox</code>	<code>(input a, b, c, d, output z);</code>
<code>// Here is where you work your // magic!</code>	
<code>endmodule</code>	

- Verilog is **CasE-SeNSitiVe**....
- Module Name : Use meaningful identifiers (~bigbox)
- Port Direction : `input`, `output`, `inout` (bidirectional)
- Port Bitwidth : `input [4:0] a` , `output [7:14] y`
- Don't forget the `__;`!

`y = 8'hFA`
number of binary bits ← 8
Value (11111010) ← hFA
h, o, d, b (radix)

Continuous Assignment (Dataflow)

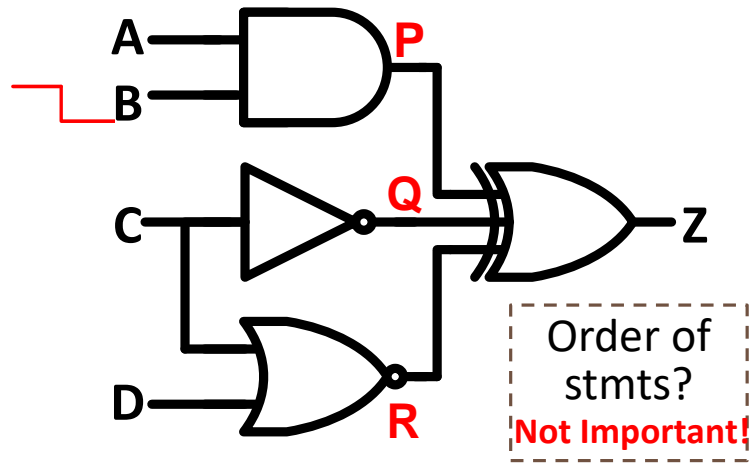assign statements are used to model combinational logic




```
module bigbox (input a, b, c, d,  
               output z);
```

```
  wire p, q, r; internal connections
```

```
    assign z = p ^ q ^ r; 1  
    assign q = ~c;         2  
    assign p = a & b;      3  
    assign r = ~(c | d);  4
```

```
endmodule
```

 

- Whenever there's an **event** on the RHS signal, expression is evaluated and assigned (Δ = prop. delay) \rightarrow *continuously monitored*
- Multiple statements can be executed in parallel (concurrently)
- **wire** is used to represent an internal connection


Useful Operators

- Boolean (bit-wise), logical, arithmetic, concatenation.
- Use brackets for readability, take note if **synthesizable*.

<div>High</div> <div>↑</div> <div>Precedence</div> <div>↓</div> <div>Low</div>	Operator	Description	Examples: a = 4'b1010, b=4'0000
	!, ~	Logical negation, Bit-wise NOT	!a = 0, !b = 1, ~a=4'b0101, ~b=4'b1111
	&, , ^	Reduction (Outputs 1-bit)	&a = 0, a=1, ^a = 0
	{ __, __ }	Concatenation	{b, a} = 8'b00001010
	{ n{ __ } }	Replication	{ 2 {a} } = 8'b10101010
	*, /, %, ,	Multiply, *Divide, *Modulus	3 % 2 = 1, 16 % 4 = 0
	+, -	Binary addition, subtraction	a + b = 4'b1010
	<< , >>	Shift Zeros in Left / Right	a << 1 = 4'b0100, a >> 2 = 4'b0010
	<, <=, >, >=	Logical Relative (1-bit output)	(a > b) = 1
	==, !=	Logical Equality (1-bit output)	(a == b) = 0 (a != b) = 1
	&, ^,	Bit-wise AND, XOR, OR	a&b = 4'b0000 a b = 4'b1010
	&&,	Logical AND, OR (1-bit output)	a&&b = 0 a b = 1
	?:	Conditional Operator	<out> = <condition> ? If_ONE : if_ZERO

Conditional Operator...

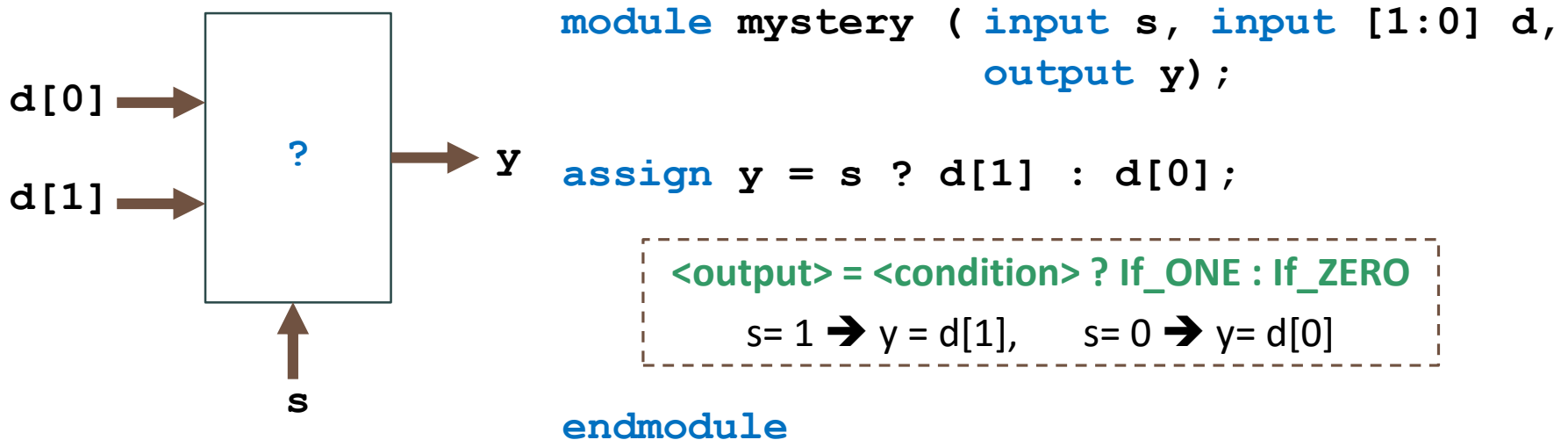The `?:` conditional operator allows us to select the output from a set of inputs based on a condition.




- This expression is evaluated whenever there is an event on any input.
- What is this block? - **Multiplexer**

Procedural Assignment : **always**

Behavioral, higher-level description of logic.

 2 assignment types : **Blocking & Non-Blocking**



```
module mux21 ( input s, input [1:0] d,  
               output reg y );
```

Anything assigned in an **always** block must be declared as type **reg**

```
always @ (s, d)
```

Conceptually, the **always** block runs once when a signal in *sensitivity list* (s,d) changes value.

```
begin
```

```
  { if ( s == 1'b0)  
    y= d[0];  
    else  
      y= d[1];
```

Statements executed sequentially & evaluated instantaneously. → Order matters!

```
end
```

```
endmodule
```

begin and **end** behave like parentheses/brackets for conditional statements.


Some notes on: `always`

- `always@(*)` includes all signals that are read in statements.
- Statements within `always` block are executed *sequentially*.
- Variables within sensitivity list are very important!
- `if--else if--else`, `case`, `for`, `while` can only be used in procedural assignments (always blocks)
- Multiple always blocks run in parallel, concurrently. (*Race)
- No ~~`assign`~~ in always blocks!
- If using `posedge` / `negedge`, all signals in sensitivity list needs to be specified with either `posedge` / `negedge`.

Registers

- Anything assigned in an `always` block must be declared as type `reg`
- In Verilog, the term register (`reg`) simply means a variable that can hold a value. (cf. `wire`)
- Values of registers can be changed instantaneously.

Equivalence...

 

```
module bigbox
  (input a,b,c,d, output z);
```

```
  wire p, q, r;
```

```
  assign q = ~c;
```

```
  assign z = p ^ q ^ r;
```

```
  assign p = a & b;
```

```
  assign r = ~(c | d);
```

```
endmodule
```

```
module bigbox
  (input a,b,c,d, output reg z);
```

```
  reg p,q,r;
```

```
  always @ ( * )
```

```
  begin
```

```
    p = a & b;
```

```
    q = ~c;
```

```
    r = ~(c | d);
```

```
    z = p ^ q ^ r;
```

```
  end
```

```
endmodule
```

Blocking & Non-blocking

Verilog supports two types of assignments within

always

= blocking assignment

- Sequential evaluation
- Immediate assignment

always @ (*)

begin

x = y; 1) Evaluate y, assign result to x
z = ~x; 2) Evaluate ~x, assign result to z
end

Behaviour	x	y	z
Initial Condition	0	0	1
y changes	0	1	1
x = y	1	1	1
z = ~x	1	1	0

<= non-blocking assignment

- Sequential evaluation
- Deferred assignment

always @ (*)

begin

x <= y; 1) Evaluate y, defer assignment
z <= ~x; 2) Evaluate ~x, defer assignment
end 3) Assign x and z with new values

Behaviour	x	y	z	Deferred
Initial Condition	0	0	1	
y changes	0	1	1	
x <= y	0	1	1	x <= 1
z <= ~x	0	1	1	z <= 1
Assignment	1	1	1	

Example

```
module example(input [2:0] A,  
               output reg [2:0] V, Z, W);
```

```
always @ (A)  
begin
```

```
    V = A | 3'b001;  
    Z <= V | 3'b100;  
    W = Z;
```


```
end  
endmodule
```

Behaviour	A	V	Z	W	Deferred
Initial Condition	000	001	101	000	
A changes	010	001	101	000	
Stmt 1	010	011	101	000	
Stmt 2	010	011	101	000	Z<=111
Stmt 3	010	011	101	101	
Assignment	010	011	111	101	

An event occurs on **A** at simulation time :

- Stmt 1 is executed and V is assigned immediately
- Stmt 2 is executed and defer assignment to Z
- Stmt 3 is executed using old value of Z.
- Z is assigned.

Verilog Time! – D-FF

 

CLK	D	Q+
↑	0	0
↑	1	1

```
module dff ( input d, clk,  
             output reg q );
```

If posedge / negedge is used in the sensitivity list, ALL signals must be used with posedge / negedge.

```
always @ (posedge clk)
```

```
begin
```


```
    q <= d;           or           q = d;
```

```
end
```


No difference since there is only one line!

```
endmodule
```

Two D Flip-Flops...

 


CLK	D	Q ⁺
↑	0	0
↑	1	1

 

Behaviour	q1	q2
Reset FFs	0	0
@ 1 st rising edge	1	0
@ 2 nd rising edge	1	1

Two D Flip-Flops... and Verilog!

 

Behaviour	q1	q2
Reset FFs	0	0
@ 1 st rising edge	1	0
@ 2 nd rising edge	1	1

```
always @ (posedge clk)
begin
```

```
q1 = d1;
q2 = q1;
```

```
end
```

Behaviour	q1	q2
Reset FFs	0	0
@ 1 st rising edge	1	1
@ 2 nd rising edge	1	1

```
always @ (posedge clk)
begin
```

```
q1 <= d1;
q2 <= q1;
```


```
end
```

Behaviour	q1	q2
Reset FFs	0	0
@ 1 st rising edge	1	0
@ 2 nd rising edge	1	1

Structural Modeling

- For modular designs, the top design is often specified as interconnected blocks.
- Two examples below demonstrate port connection by position / name.
 
```
module mymodule (input a, b, output x);  
...  
endmodule
```



Port Connection by Position

```
module ourmodule (input sw1, sw2,  
                  output led1, led2);  
  
    mymodule M1 (sw1, sw2, led1);  
    yourmodule M2 (sw1, sw2, led2);  
  
endmodule
```

```
module yourmodule (input c, d, output z);  
...  
endmodule
```

Port Connection by Name

```
module ourmodule (input sw1, sw2,  
                  output led1, led2);  
  
    mymodule M1 ( .a (sw1),  
                  .b (sw2),  
                  .x (led1) );  
  
    yourmodule M2 ( .z (led2),  
                   .c (sw1),  
                   .d (sw2) );  
  
endmodule
```


Basic Guidelines...

#1: When modeling sequential logic, use nonblocking assignments.

#2: When modeling simple combinational logic, use continuous assignments (assign).

#3: When modeling complex combinational logic, use blocking assignments in an always block.

#3: When modeling both sequential and combinational logic within the same always block, use nonblocking assignments.

#4: Do not mix blocking and nonblocking assignments in the same always block.

#5: Do not make assignments to the same variable from more than one always block.

Summary

- Operators (\sim , $*$, $/$, $+$, $-$, $\&$, $^$, $|$)
- Continuous assignments (**assign**)
- Procedural assignments (**always**)
 - Blocking assignment (**=**)
 - Non-blocking assignment (**<=**)
- Modeling of multiple D Flip-flops
- Structural Modeling

Try this!

`assign` is used for

In continuous assignments,
the code is executed

The code in the `always`
block is executed when


`always` is used for

`<=` is a

`endmodule` is always
paired with

The sensitivity list follows
the

Code in `always` block is
executed

 

`always @.`

when any RHS signal
changes

module

sequentially.

non-blocking procedural
assignment.

continuous assignments.

procedural assignments.

a signal in the sensitivity
list changes.

Verilog : Simulation & Synthesis




SELF - READING

What is Simulation?


 
```
module savetheworld (input a1, ... z1,  
                    output a2, ..., z2);  
    .....  
    .....  
    .....  
endmodule
```



How do we know our design actually works?

- Functional Simulation
(Xilinx)

Method


- Designer applies input values to the code
- Simulator produces corresponding outputs in truth tables / timing diagrams
- Simulators usually assume negligible propagation gate delays.

Verilog Code

```
module  
    .....  
    .....  
endmodule
```

Test Bench
 
```
call module  
a1=9;  
b1=1;  
//wait for 10u  
#10  
b1=0;
```



What is Synthesis?

Now that our design is working,
time to save the world.



```
module savetheworld
(input a1,...z1, output a2,...,z2);
.....
count <= count + 1 ;
endmodule
```

Synthesis :

1) Translation

- Code is transformed into hardware (gates & wires).


2) Optimization

- Minimizes the amount of hardware required.


3) Mapping

- Implements hardware on target device.

Translation + Optimization

 

Mapping

 

"This looks like a NOT gate. My FPGA can do some of these..."

Summary

- Operators (\sim , $*$, $/$, $+$, $-$, $\&$, $^$, $|$)
- Continuous assignments (**assign**)
- Procedural assignments (**always**)
 - Blocking assignment (**=**)
 - Non-blocking assignment (**<=**)
- Modeling of multiple D Flip-flops
- Structural Modeling