

(T)EE2026 DIGITAL DESIGN

TUTORIAL 4: BOOLEAN ALGEBRA AND MINIMIZATION

GU JING (DR)


ELEGUJI@NUS.EDU.SG

Summary of Lecture 5: Gate-level Design & Minimization

- Gate-level logic design**

- Simplify the Boolean function
- Implement the simplified Boolean function using logic gates, minimizing the gate count

- Karnaugh Map (K-Map)**

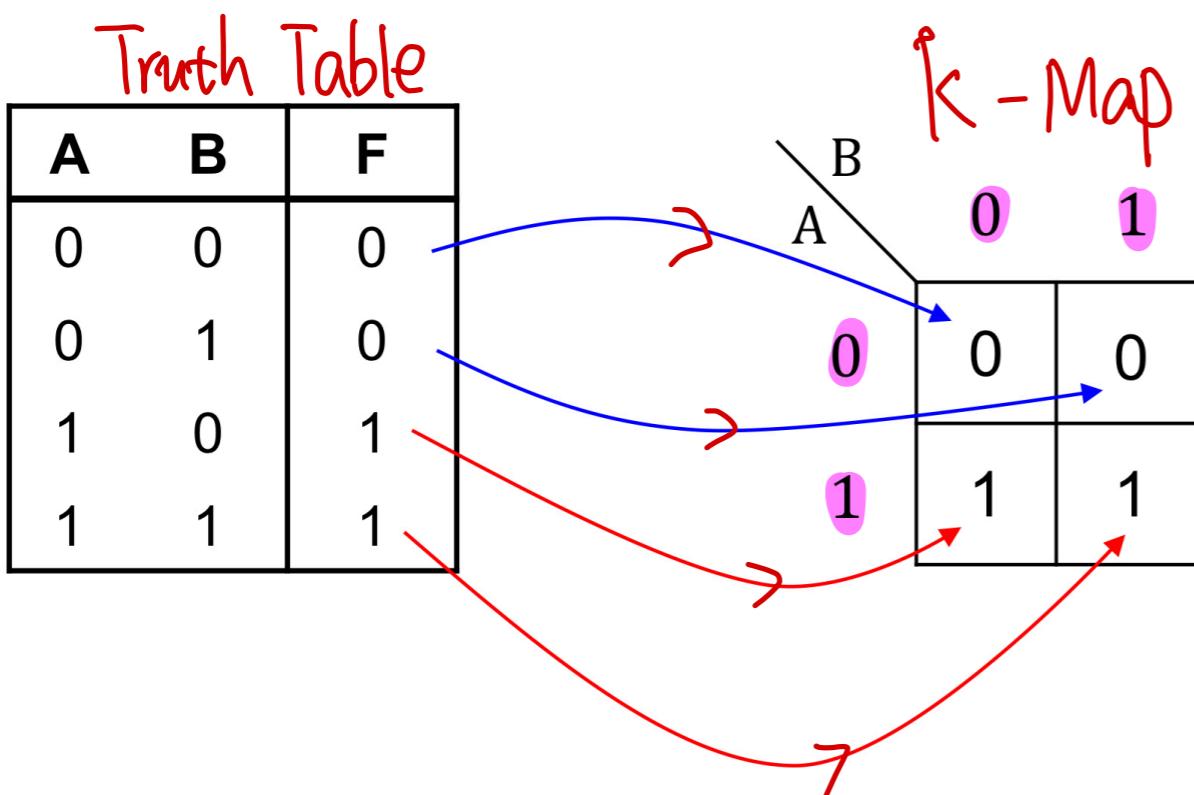

Three-variable K-map


00	01	11	10
$\bar{B}\bar{C}$	$\bar{B}C$	BC	$B\bar{C}$
$\bar{A}\bar{B}\bar{C}$	$\bar{A}\bar{B}C$	$\bar{A}BC$	$\bar{A}B\bar{C}$
$A\bar{B}\bar{C}$	$A\bar{B}C$	ABC	$AB\bar{C}$

Four-variable K-map

00	01	11	10	
CD	AB			
00	0000	0001	0011	0010
01	0100	0101	0111	0110
11	1100	1101	1111	1110
10	1000	1001	1011	1010

Summary of Lecture 5: Gate-level Design & Minimization

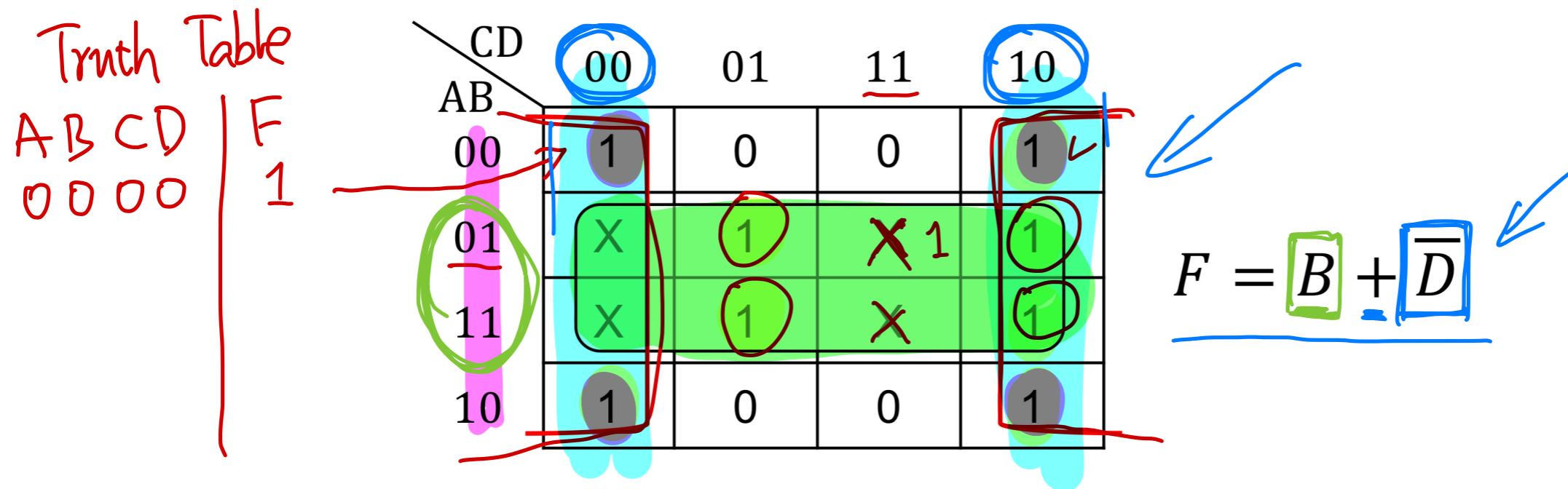
- Simplification using K-map for SOP minimization group "I"



- Group the squares that only contains “1”, or don’t care condition “X”
- Groups must be either horizontal or vertical (diagonal is invalid)
- Group size is always 2^n , that is, 2, 4, 8, ...
- Group should be as large as possible (contains as many as squares with “1” as possible)
- Each square with “1” must be part of a group if possible
- Simplified term retains those variables that don’t change value
- Variables that change value in the group are eliminated

Summary of Lecture 5: Gate-level Design & Minimization

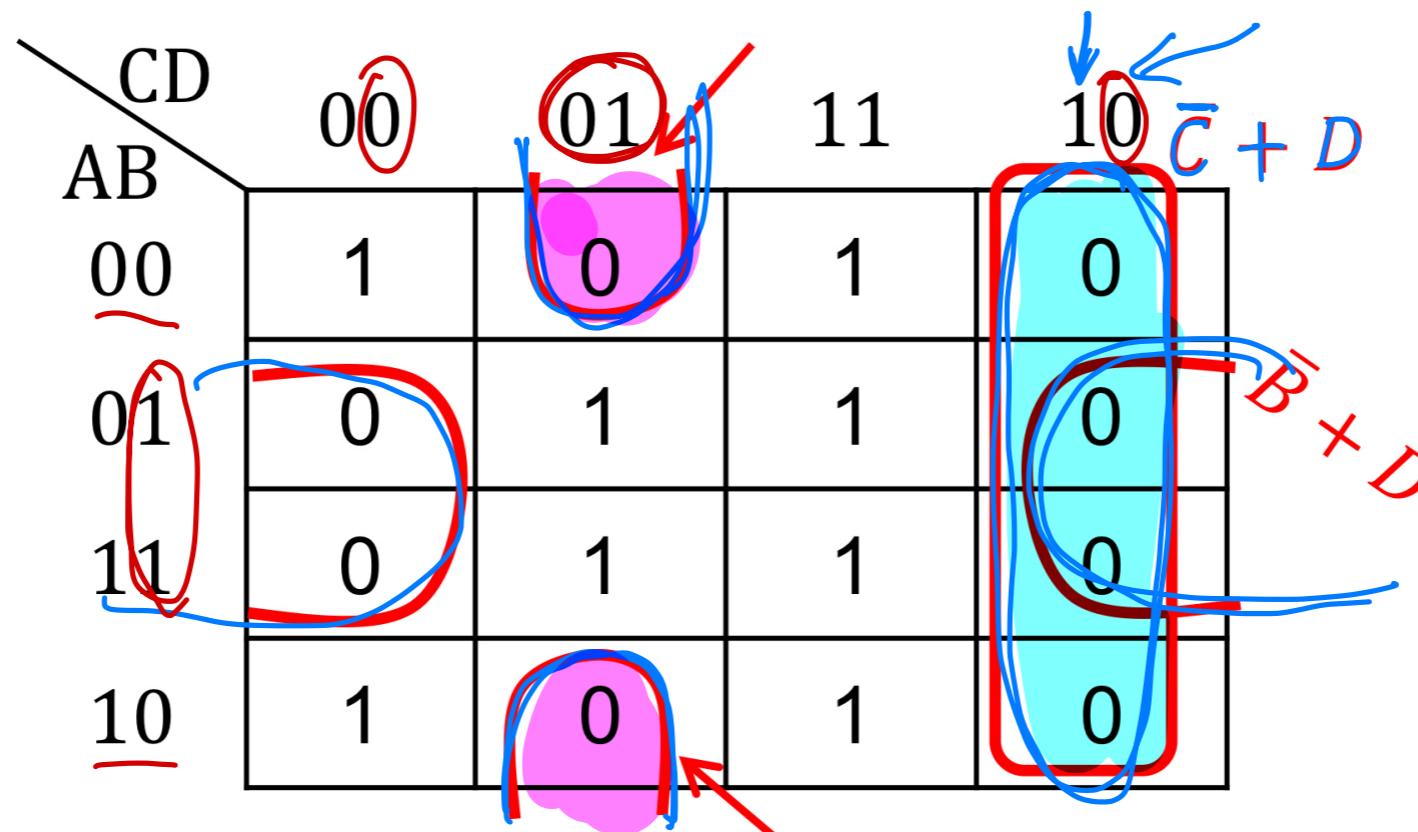- Simplification using K-map for POS minimization



$$F = \underbrace{(B + C + \bar{D})}_{\text{red}} \cdot \underbrace{(\bar{C} + D)}_{\text{blue}} \cdot \underbrace{(\bar{B} + D)}_{\text{red}}$$

- Group the squares that only contains “0”
- Form an OR term (sum) for each group, instead of a product
- Value “1”, instead of “0”, represent complement of the variable
- Follow similar grouping rules for SOP

Summary of Lecture 5: Gate-level Design & Minimization

- **Minimal SOP (MSOP): group “1”s in most efficient way**


CD \ AB	00	01	11	10
00	1	0	1	1
01	1	0	1	0
11	1	1	1	1
10	0	0	0	0

CD \ AB	00	01	11	10
00	0	0	1	0
01	1	0	1	1
11	1	1	1	1
10	0	0	1	0


CD \ AB	00	01	11	10
00	1	0	0	1
01	1	1	1	1
11	1	0	1	0
10	1	0	1	1

Summary of Lecture 5: Gate-level Design & Minimization

- **NAND only Implementation**

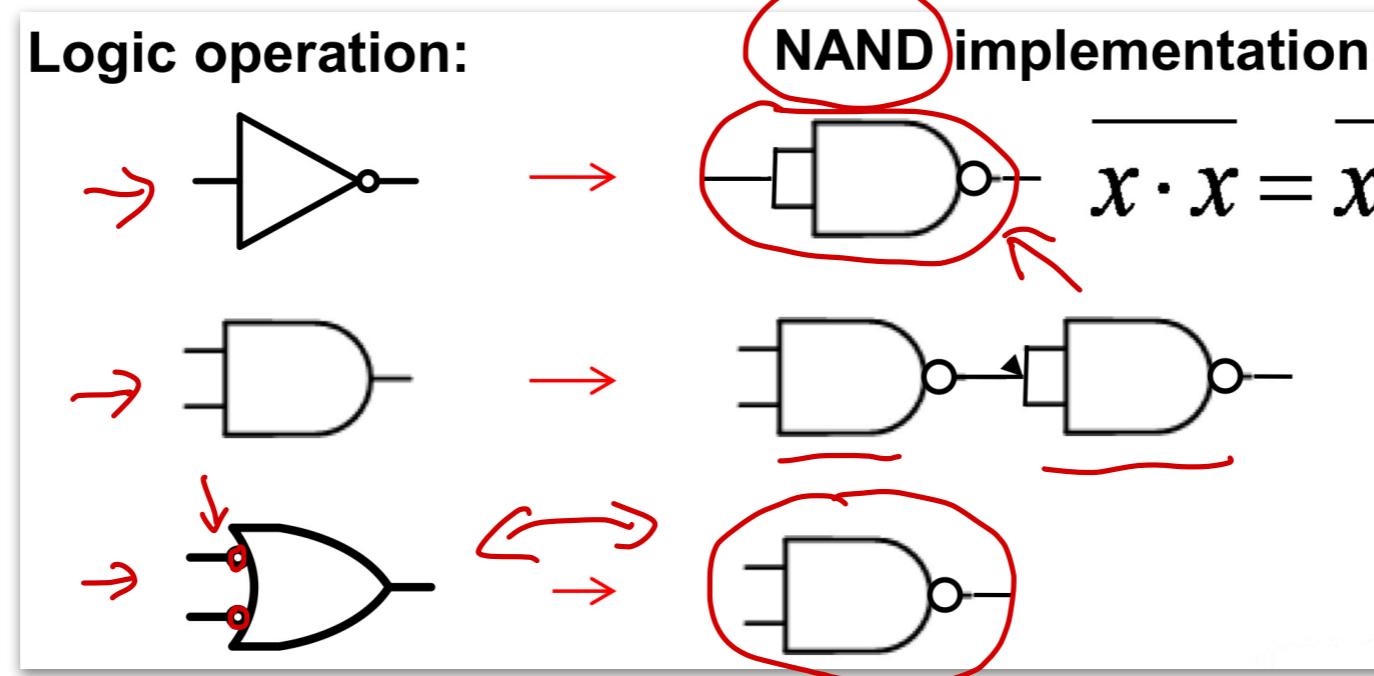

- **NOR only Implementation**

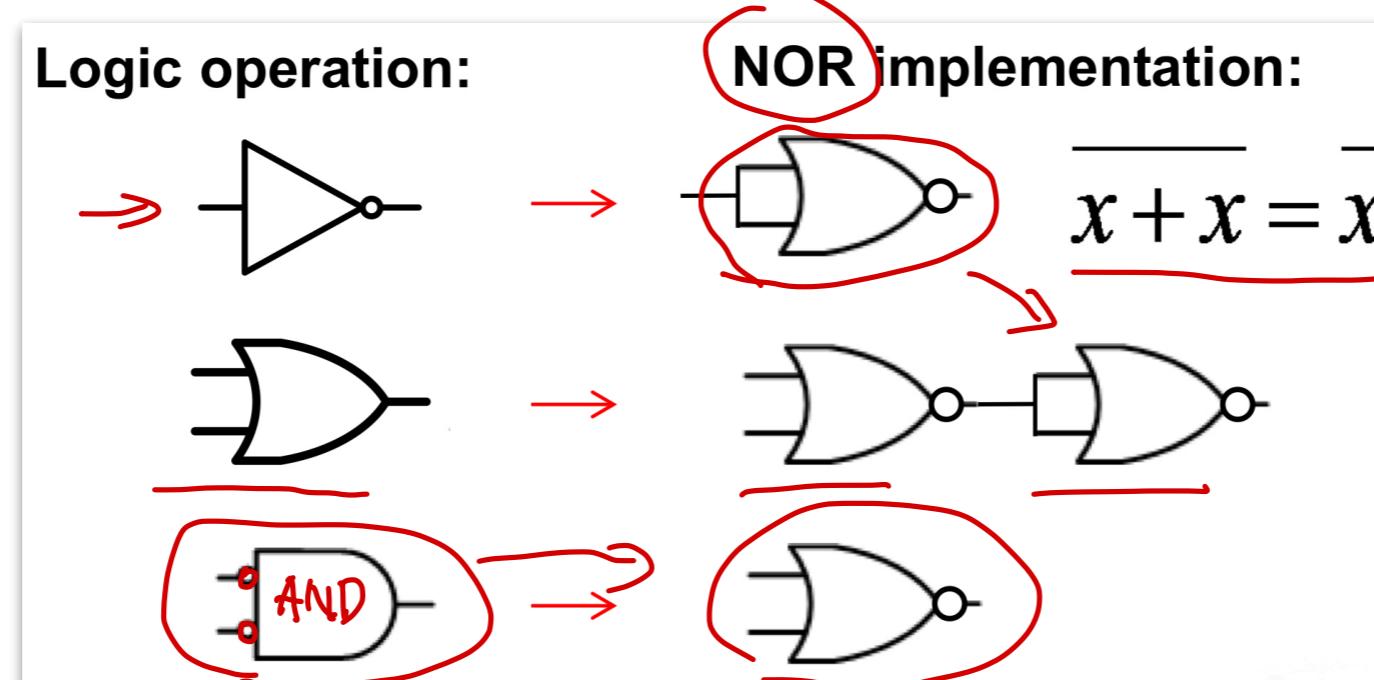


Q1. A switching circuit has four inputs as shown. A and B represent the first and second bits of a binary number N_1 . C and D represent the first and second bits of a binary number N_2 . The output is to be 1 only if the product $N_1 \times N_2$ is less than or equal to 2.

(a) Write the truth table for the system.

(b) Write the canonical SOP and POS expressions for F.
minterms *maxterms* ($A\bar{B} + \bar{B}C + \bar{D}$)

(c) Draw a Karnaugh-map (K-map) for the function F.

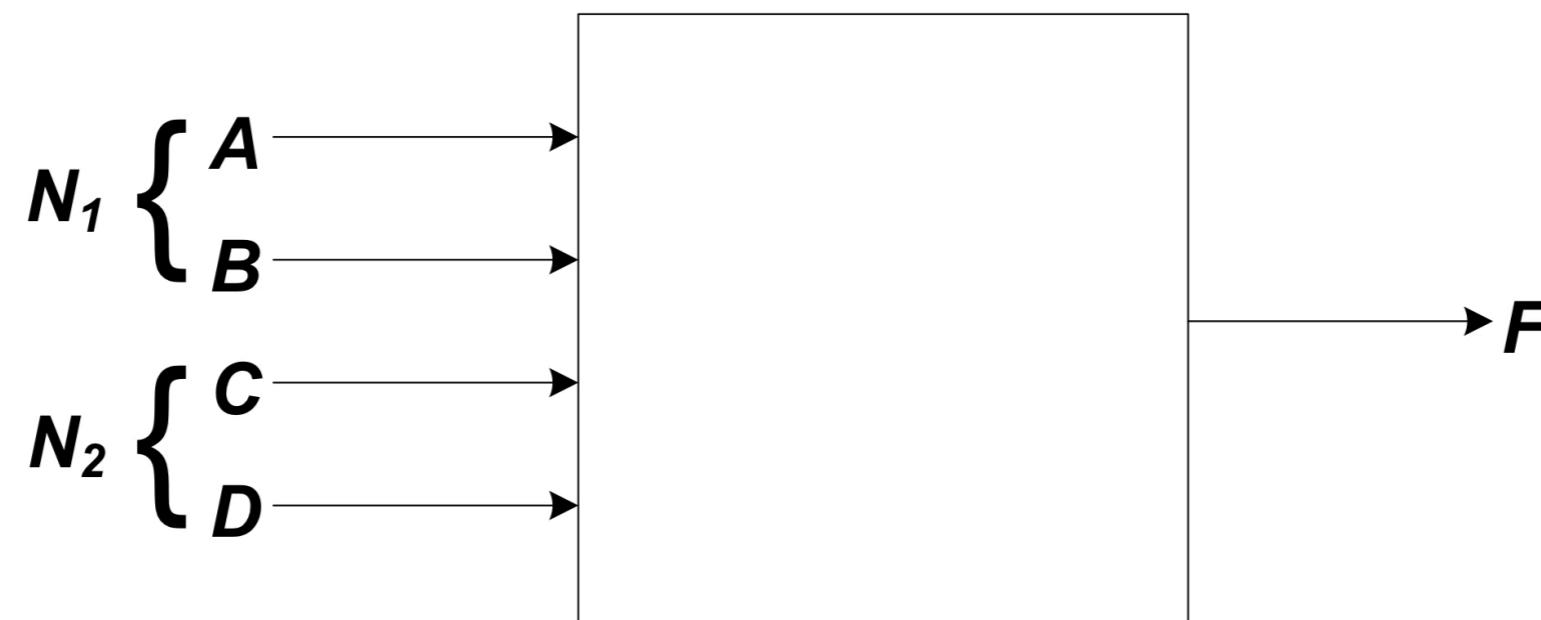
(d) From the K-map, derive a simplified SOP expression for F. (Hint: Use groups of only size 4.)



(T)EE2026 Tutorial 4: Boolean Algebra and Minimization

Q1 Ans: (a)
^{b-d}

A	B	C	D	F
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	0
1	0	1	1	0
1	1	0	0	1
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

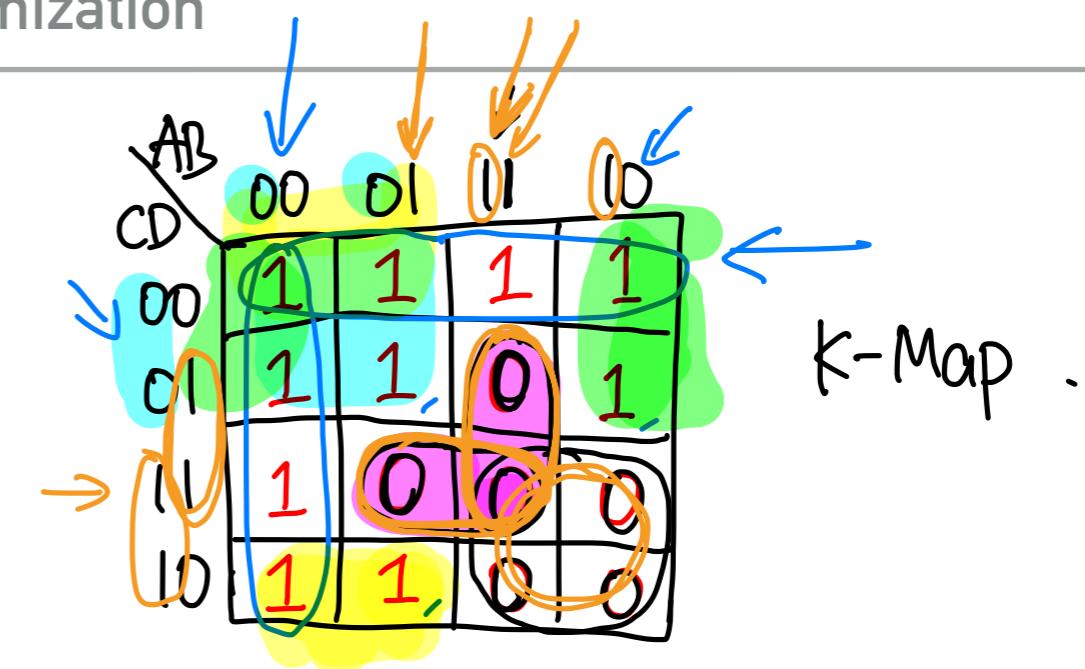

SOP (check all "1"s)

$$F = \bar{A}\bar{B} + \bar{C}\bar{D} + \bar{A}\bar{C} + \bar{B}\bar{C} + \bar{A}\bar{D}$$

POS (check all "0"s)

$$F = (\bar{A} + \bar{C}) \cdot (\bar{A} + \bar{B} + \bar{D}) \cdot (\bar{B} + \bar{C} + \bar{D})$$

Q1 Ans: (a)

A	B	C	D	F
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	0
1	0	1	1	0
1	1	0	0	1
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

(b)

Canonical SOP (check “1”s):

$$F = \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}C\bar{D} + \bar{A}\bar{B}CD + \\ \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}C\bar{D} + \bar{A}\bar{B}CD + \\ A\bar{B}\bar{C}\bar{D} + AB\bar{C}\bar{D}$$

Canonical POS (check “0”s):

$$F = (A+\bar{B}+\bar{C}+\bar{D}) \cdot (\bar{A}+B+\bar{C}+D) \cdot \\ (\bar{A}+B+\bar{C}+\bar{D}) \cdot (\bar{A}+\bar{B}+C+\bar{D}) \cdot (\bar{A}+\bar{B}+\bar{C}+D) \cdot \\ (\bar{A}+\bar{B}+\bar{C}+\bar{D})$$

Q1 Ans: (c)

A	B	C	D	F
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	0
1	0	1	1	0
1	1	0	0	1
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0



	AB CD	00	01	11	10
00	1	1	1	1	1
01	1	1	0	1	1
11	1	0	0	0	0
10	1	1	0	0	0

Q1 Ans: (d)


AB CD	00	01	11	10
00	1	1	1	1
01	1	1	0	1
11	1	0	0	0
10	1	1	0	0

SOP (check all “1”s):

AB CD	00	01	11	10
00	1	1	1	1
01	1	1	0	1
11	1	0	0	0
10	1	1	0	0


POS (check all “0”s):

Q1 Ans: (d)

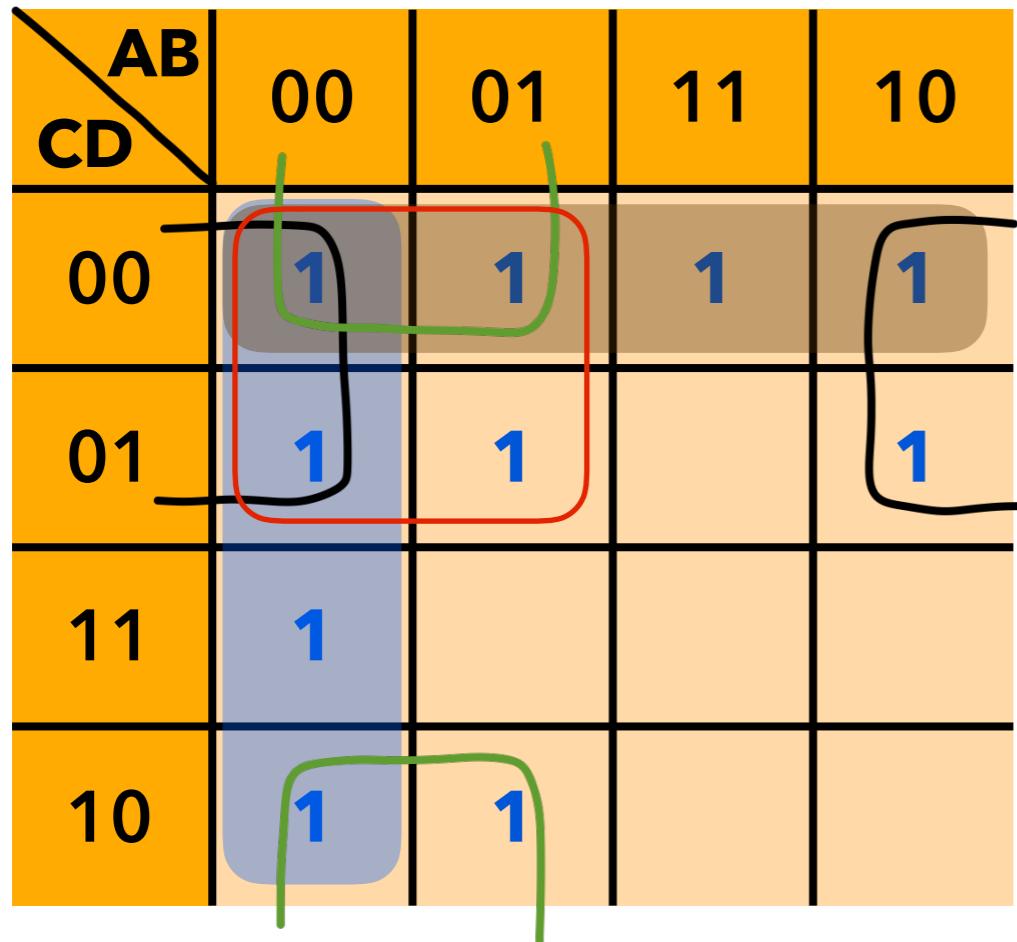

SOP (check all “1”s):
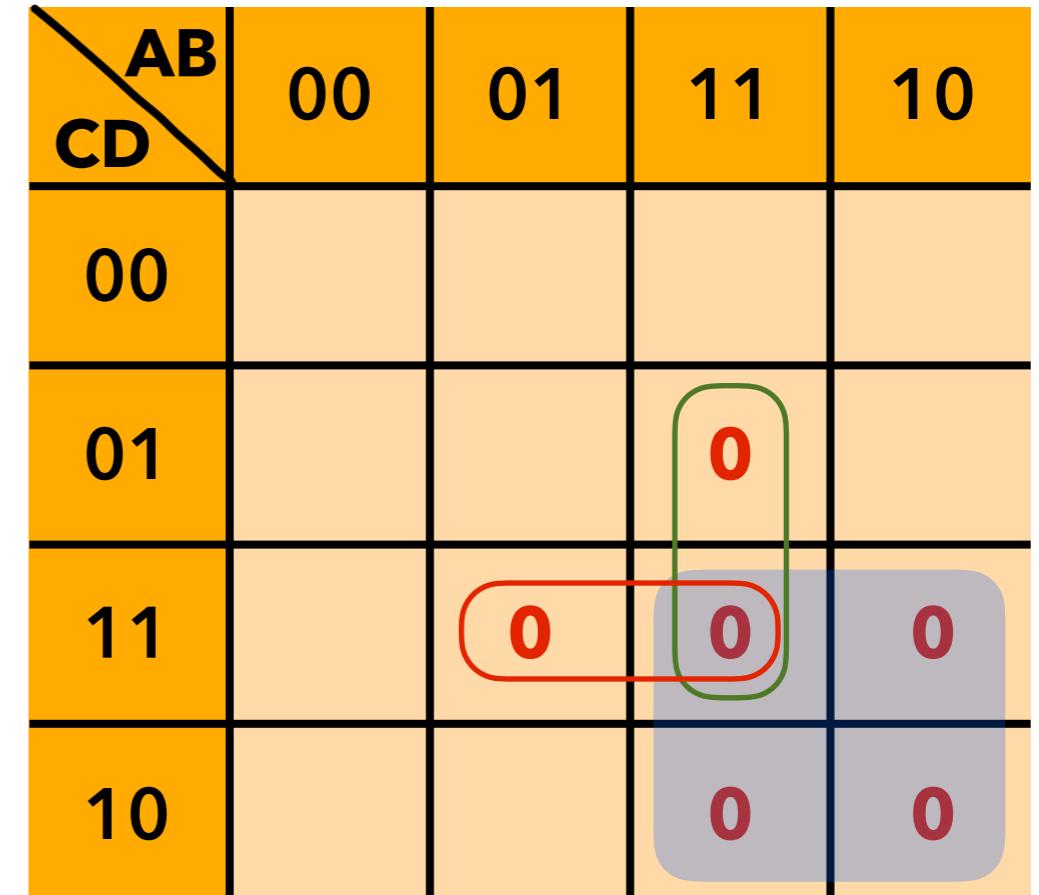
$$Z_{MSOP} = \bar{A}\bar{B} + \bar{C}\bar{D} + \bar{A}\bar{C} + \bar{A}\bar{D} + \bar{B}\bar{C}$$



POS (check all “0”s):

$$Z_{MPOS} = (\bar{A}+\bar{C})(\bar{A}+\bar{B}+\bar{D})(\bar{B}+\bar{C}+\bar{D})$$

Q2. A bank vault has three locks with a different key for each lock. Each key is owned by a different person. To open the door, at least two people must insert their keys into the assigned locks. The signal lines A, B and C are 1 if there is a key inserted into lock 1, 2 or 3, respectively. Write an equation for the variable Z which is 1 if and only if the door should open.

- (a) Write the truth table for the system.
- (b) Write the canonical SOP and POS expressions for Z.
- (c) Draw a Karnaugh-map (K-map) for the function Z.
- (d) From the K-map, derive a simplified SOP expression for Z.

(T)EE2026 Tutorial 4: Boolean Algebra and Minimization

Q2 Ans:

A	B	C	F
0	0	0	0 ←
0	0	1	0 ←
0	1	0	0 ←
0	1	1	1 ←
1	0	0	0 ←
1	0	1	1 ←
1	1	0	1 ←
1	1	1	1 ←

Canonical SOP (check "1")


$$F = \bar{A}\bar{B}C + A\bar{B}\bar{C} + A\bar{B}C + ABC$$

Canonical POS (check "0"s)

$$F = (\bar{A}+B+C) \cdot (\bar{A}+\bar{B}+\bar{C}) \cdot (\bar{A}+\bar{B}+C)$$

$$\cdot (\bar{A}+B+C)$$

k-Map

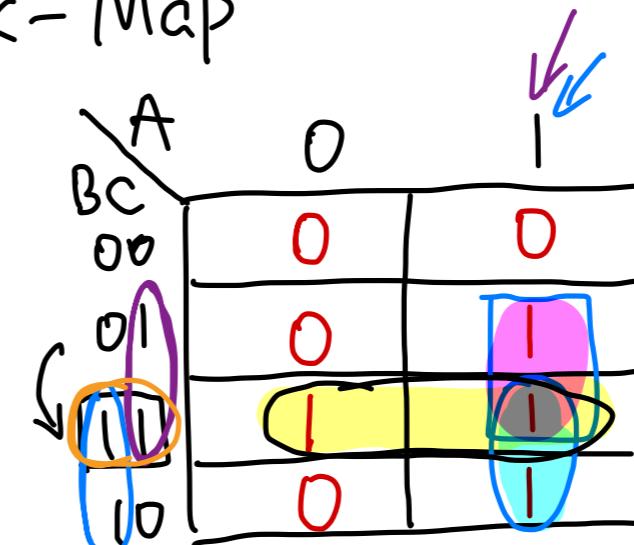


minimal SOP:

$$F = AB + AC + \underline{+ BC}$$

Q2 Ans:

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

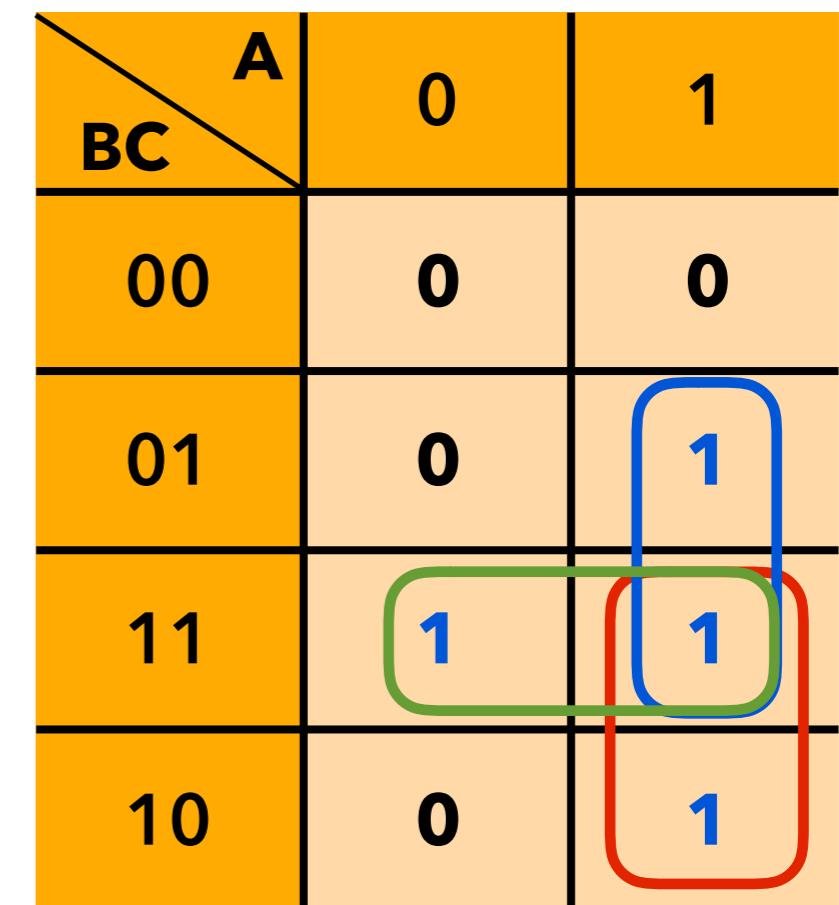

$$Z_{SOP} = \bar{A}\bar{B}C + A\bar{B}C + A\bar{B}\bar{C} + ABC$$

$$Z_{POS} = (A+B+C)(A+B+\bar{C})(A+\bar{B}+C)(\bar{A}+B+C)$$

$$F = AC + BC + AB$$

Q3. Use K-maps to obtain an MSOP and an MPOS for each of the following functions:

(a) $Z = \overline{A}\overline{B}\overline{C}D + \overline{A}B\overline{C}D + A\overline{B}\overline{C}D + A\overline{B}\overline{C}\overline{D} + A\overline{B}CD$ with don't care for ABCD
= 1010

(b) $Z = (\overline{A} + B + \overline{C})(A + B + \overline{C})$ with don't cares for ABC = 111 and 110

(c) $f(x_1, L, x_4) = \sum m(0, 4, 5, 6, 7) + D(1, 12, 13, 14, 15)$, where $m()$ is the set of minterms for which $f=1$ and $D()$ is the set of don't cares. For example, $m(2)$ is the minterm corresponding to $x_1x_2x_3x_4 = 0010$ (this alternate shorthand notation is often used to express SOPs).

Canonical format

$\overline{ABCD} = 0001$

$\overline{0101}$

$\overline{1101}$

$\overline{1001}$

$\overline{1000}$


SOP

Q3(a). $Z = \overline{ABCD} + \overline{ABC}\overline{D} + ABC\overline{D} + A\overline{B}\overline{C}\overline{D} + A\overline{B}\overline{C}D$ with don't care for

$ABCD = 1010$

MPOS MSOP

\diagdown AB	00	01	11	10
CD	00	01	11	10
00	0	0	0	1
01	1	1	1	1
11	0	0	0	0
10	0	0	0	X0

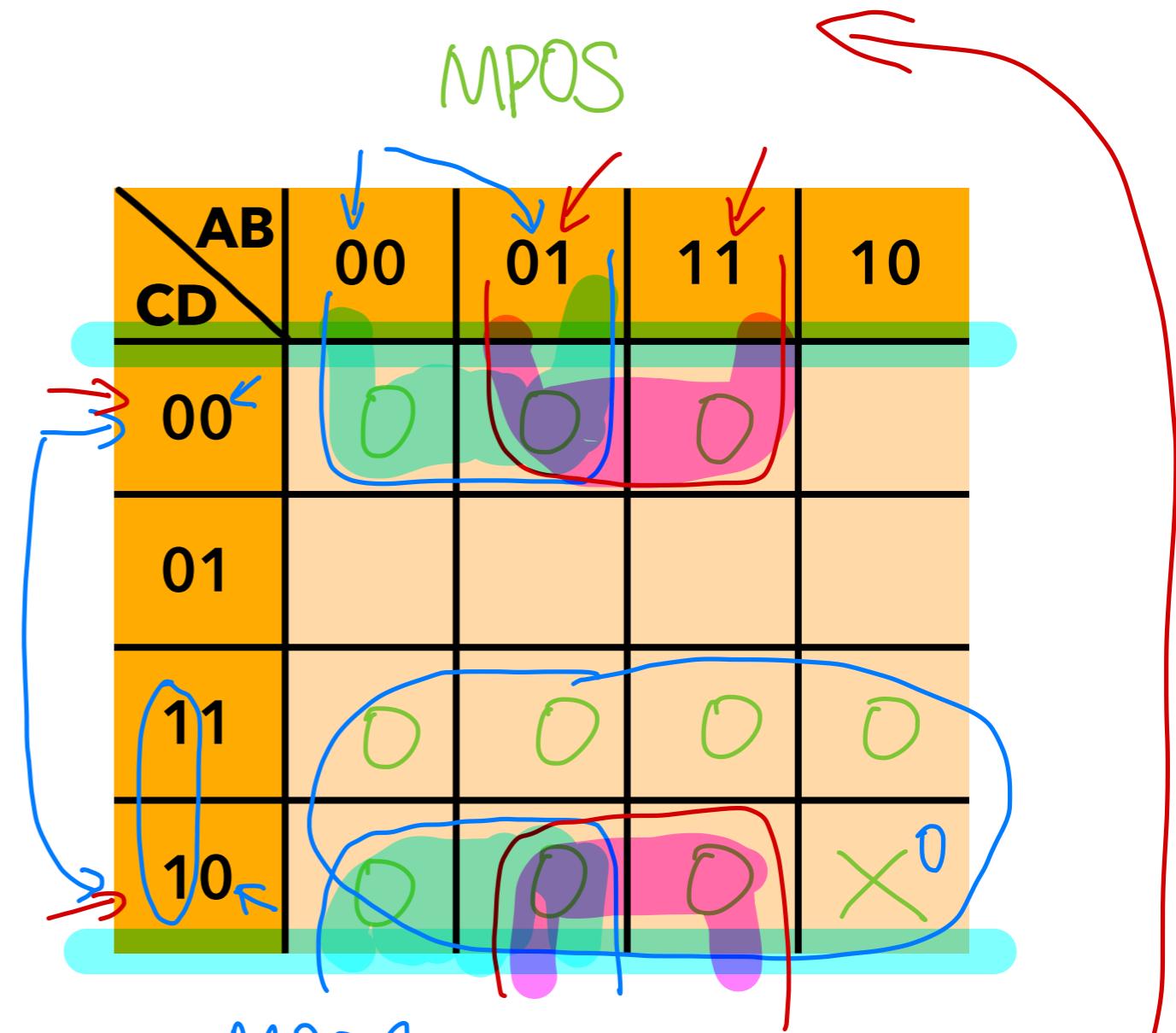

MSOP: ("i"s)

$Z = \overline{CD} + A\overline{B}\overline{C} *$

MPOS :

$Z = \underline{\overline{C}} \cdot (A+D) \cdot (\overline{B}+D) *$

Q3(a). $Z = \overline{A}\overline{B}\overline{C}D + \overline{A}B\overline{C}D + A\overline{B}\overline{C}D + A\overline{B}\overline{C}\overline{D} + A\overline{B}\overline{C}D$ with don't care for $ABCD = 1010$

AB	00	01	11	10
CD				
00				1
01	1	1	1	1
11				
10				x

AB	00	01	11	10
CD				
00	0	0	0	
01				
11	0	0	0	0
10	0	0	0	x

$$Z = \overline{A}\overline{B}\overline{C} + \overline{C}D$$

$$Z = \overline{C}(\overline{B}+D)(A+D)$$

(T)EE2026 Tutorial 4: Boolean Algebra and Minimization

Q3(b). $Z = (\overline{A} + B + \overline{C})(A + B + \overline{C})$ with don't cares for $ABC = 111$ and 110

$$\begin{array}{cccc} \uparrow & \downarrow & \downarrow & \downarrow \\ 0 & A=1 & B=0 & C=1 \\ \end{array}$$

$\overbrace{\quad\quad\quad}^{\text{ABC}=001}$

	A	0	1
BC	00	1	1
	01	0	0
	11	1	X
→	10	1	X

The Karnaugh map shows minterms 10, 11, and 00. The minterm 10 is circled in red. The minterms 11 and 00 are grouped together by a blue oval.

MSOP: (check "1"s)

$$Z = B + \overline{C} *$$

→ $Z = (B + \overline{C}) *$

	A	0	1
BC	00		
	01	0	0
	11		X
→	10		X

The Karnaugh map shows minterms 01, 11, and 10. The minterms 01 and 11 are circled in red. The minterm 10 is circled in blue.

MPOS: (check "0"s)

$$Z = (B + \overline{C}) *$$

Q3(b). $Z = (\overline{A} + B + \overline{C})(A + B + \overline{C})$ with don't cares for ABC = 111 and 110

\backslash	A	0	1
BC			
00			
01	0	0	
11		X	
10		X	

\backslash	A	0	1
BC			
00		1	1
01			
11	1	X	
10	1	X	

$$Z = B + \overline{C}$$

$$Z = B + \overline{C}$$

$$m(0) \quad m(4) = \underline{0100} \quad m(5) = \underline{0101} \quad m(7) = 0111$$

(T)EE2026 Tutorial 4: Boolean Algebra and Minimization

~~$m(0)$~~ $m(4) = \underline{0100}$ $m(5) = \underline{0101}$ $m(7) = 0111$
 ~~$m(1)$~~ $m(6) = 0110$ $m(12) = 1100$
 ~~$m(2)$~~ $m(13) = 1101$

Q3(c). $f(x_1, L, x_4) = \sum m(0, 4, 5, 6, 7) + D(1, 12, 13, 14, 15)$, where $m()$ is the set of minterms for which $f=1$ and $D()$ is the set of don't cares. For example, $m(2)$ is the minterm corresponding to $x_1x_2x_3x_4 = \underline{\underline{0010}}$ (this alternate shorthand notation is often used to express SOPs).

$\cancel{x_1x_2}$	00	01	11	10
$\cancel{x_3x_4}$	00	01	11	10
00	1	1	X	0
01	X	1	X	0
11	0	1	X	0
10	0	1	X	0

$\cancel{x_1x_2}$	00	01	11	10
$\cancel{x_3x_4}$	00	01	11	10
00			X	0
01		X		0
11			X	0
10			X	0

MSOP: (check "1"s)

MPOS: (check "0"s)

$$f = X_2 + \bar{X}_3 \cdot \bar{X}_1 \Leftrightarrow f = (\bar{X}_1) \cdot (X_2 + \bar{X}_3)$$

Q3(c). $f(x_1, L, x_4) = \sum m(0, 4, 5, 6, 7) + D(1, 12, 13, 14, 15)$, where $m()$ is the set of minterms for which $f=1$ and $D()$ is the set of don't cares. For example, $m(2)$ is the minterm corresponding to $X_1X_2X_3X_4 = 0010$ (this alternate shorthand notation is often used to express SOPs).

$\cancel{X_1X_2}$	00	01	11	10
$\cancel{X_3X_4}$	00	1 1	X	
00	X	1	X	
01		1	X	
11		1	X	
10		1	X	


$\cancel{X_1X_2}$	00	01	11	10
$\cancel{X_3X_4}$	00			X 0
00	X		X	0
01		X		0
11		0		X 0
10	0		X	0

$$Z = X_2 + \overline{X}_1\overline{X}_3$$

$$Z = \overline{X}_1 (X_2 + \overline{X}_3)$$

3 or more "1's" $\rightarrow Z=1$


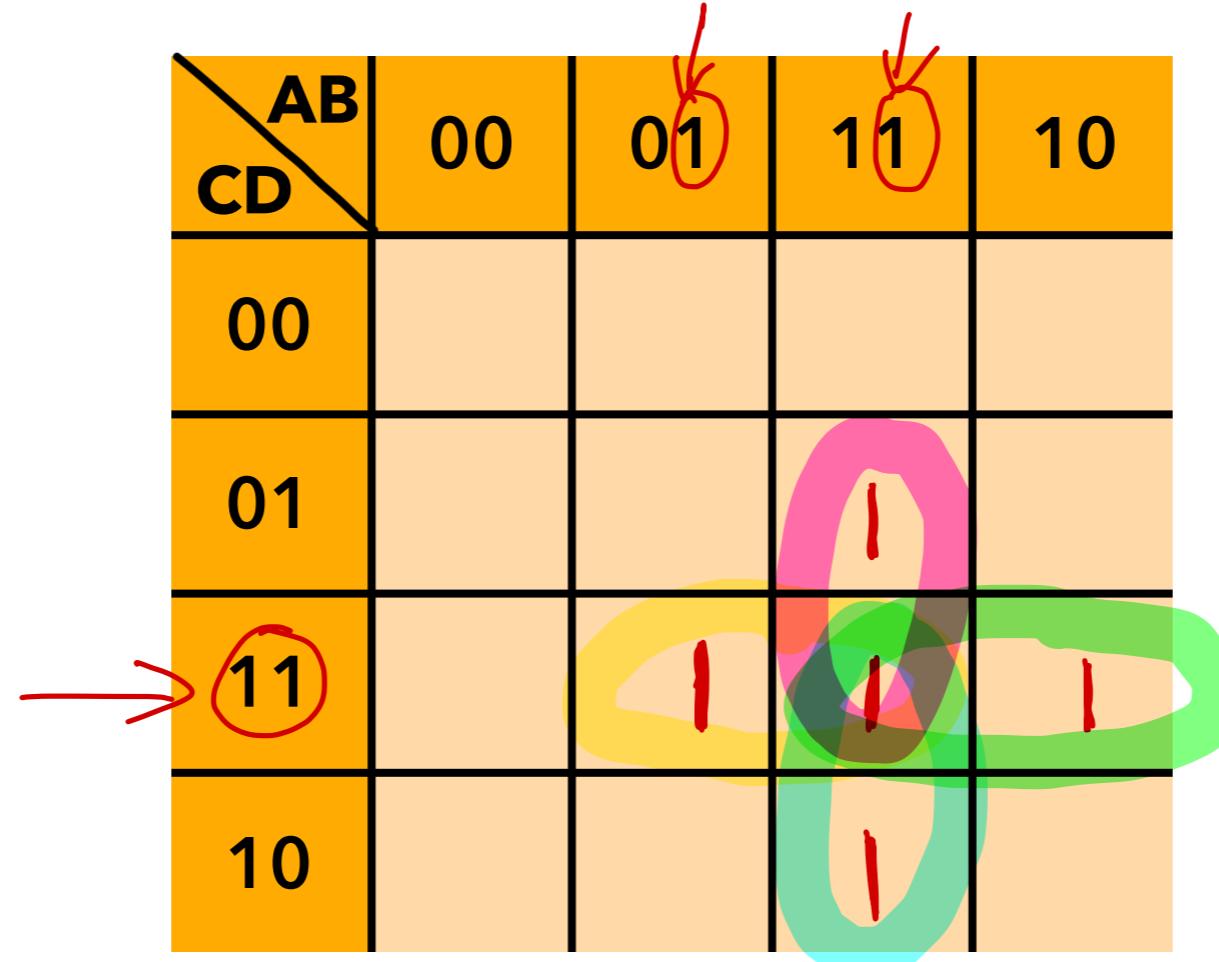
Q4. A combinational circuit has four inputs A, B, C and D and an output Z. The output is asserted whenever three or more of the inputs are asserted, otherwise the output is de-asserted. Find an MSOP expression for Z. Design combinational circuits using only 74'04 inverters, 74'00 2-input NAND gates and 74'10 3-input NAND gates. Assume that A, B and Z are active high signals, while C and D are active low signals. Use alternate gate representations for clarity of circuit diagrams.



MSOP:

$$Z = \underline{ABD} + \underline{ACD} + \underline{ABC} + \underline{BCD}$$
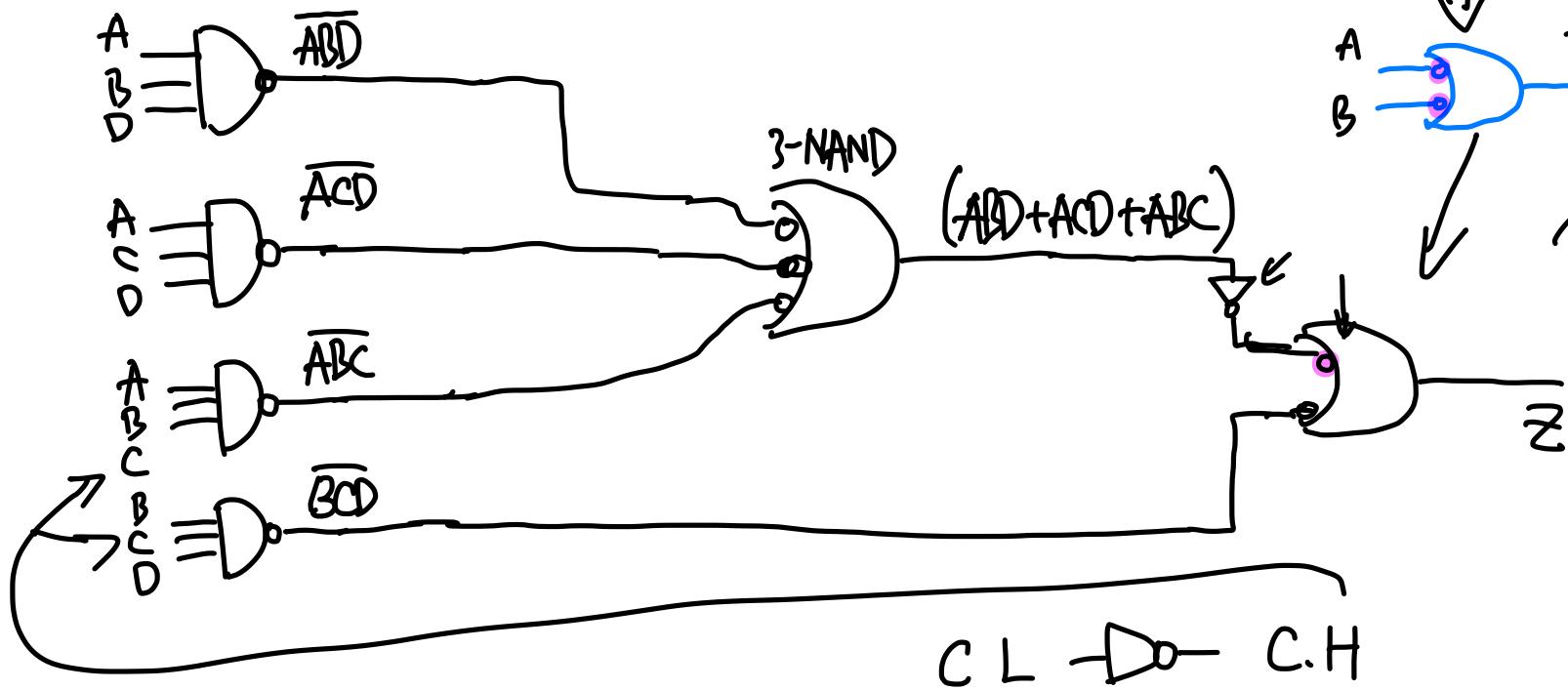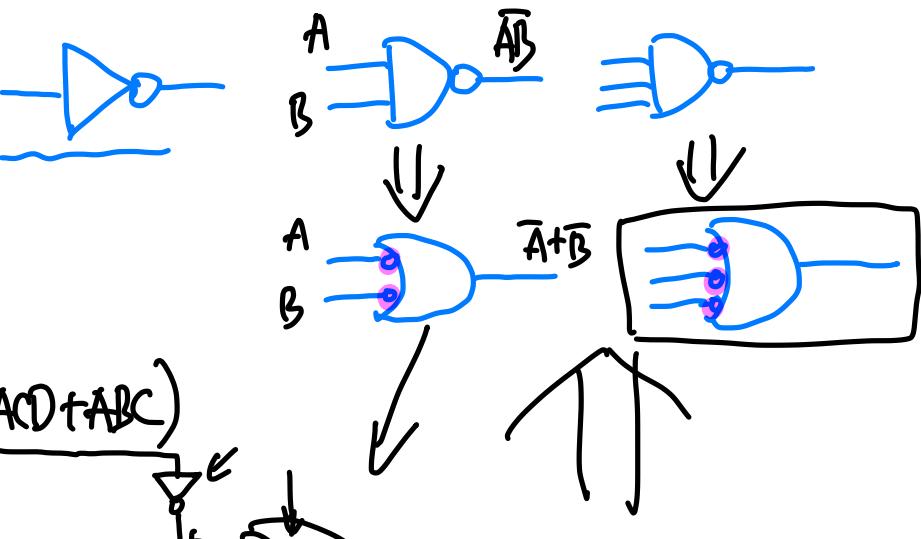
$$Z = \overline{ABD} + \overline{ACD} + \overline{ABC} + \overline{BCD}$$




C & D active low

Q4 Ans.

AB	00	01	11	10
CD	00			
00				
01			1	
11		1	1	1
10			1	

$$Z = ABD + ACD + ABC + BCD$$

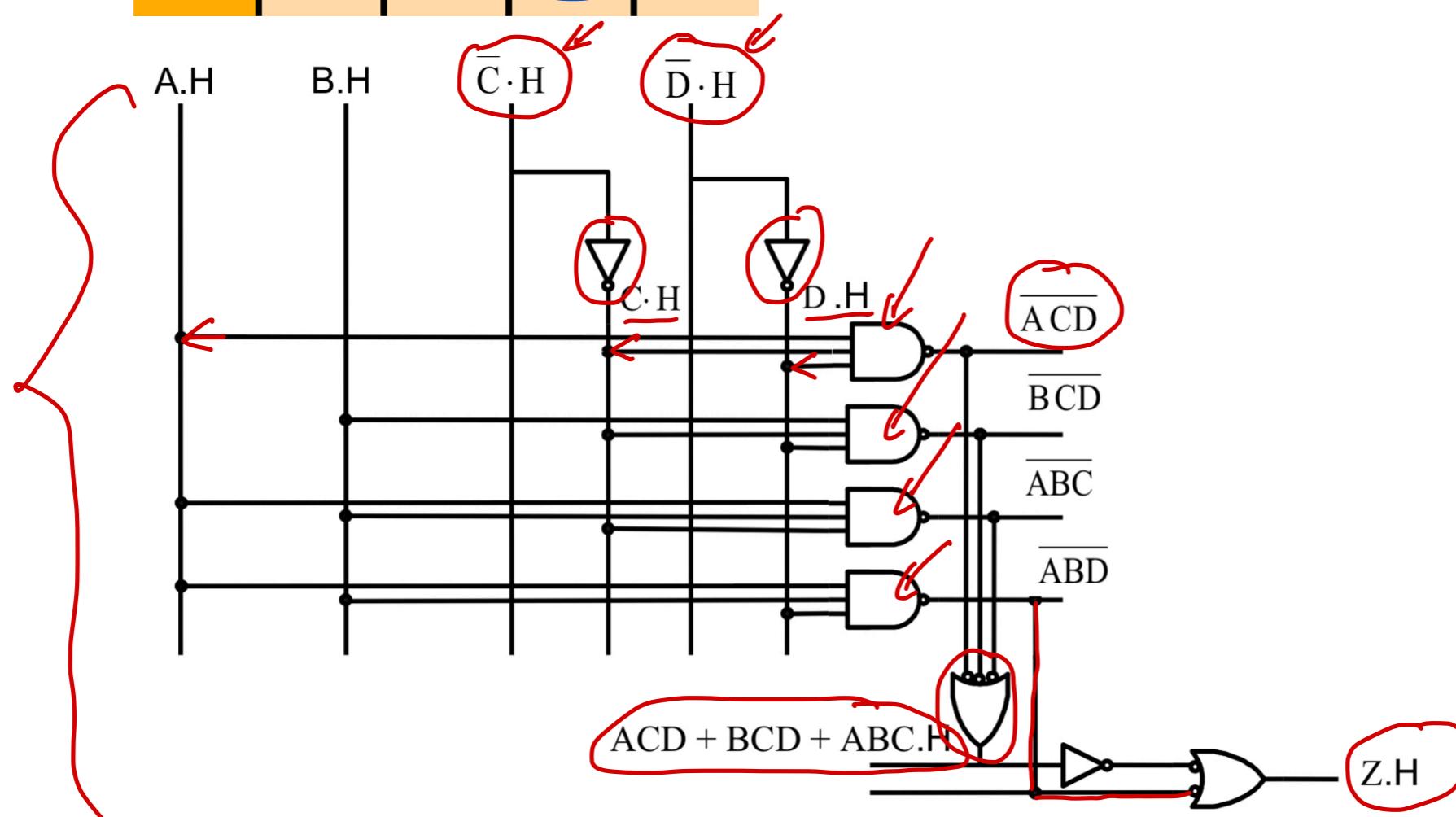

$$\underline{Z.H = ACD + BCD + ABC + ABD.H}$$

THE END

For Consultation: eleguji@nus.edu.sg

Office: E4-03-10