
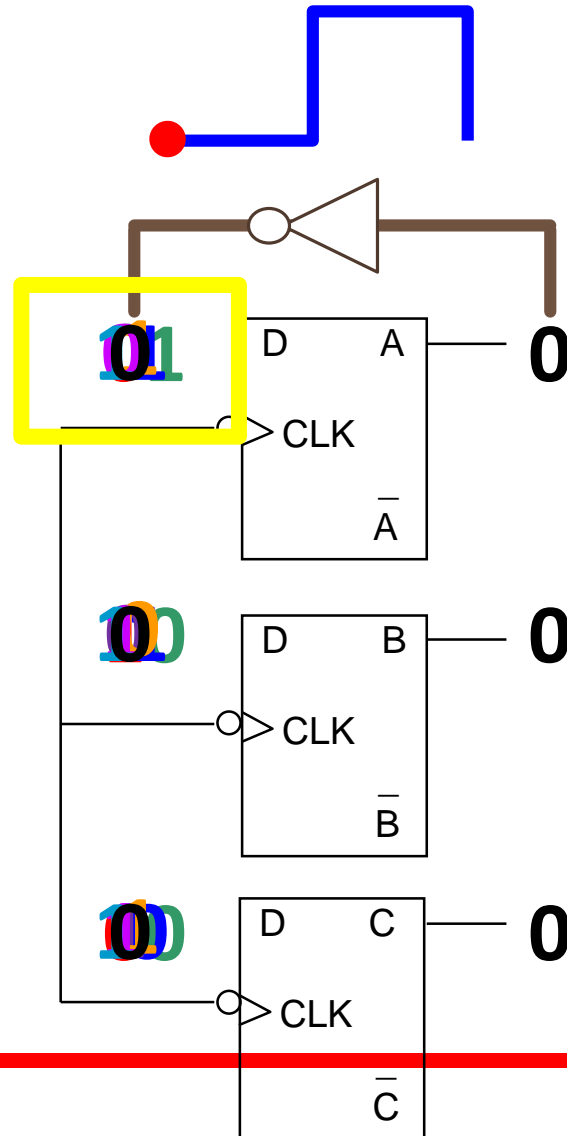


# Counter Animation


---

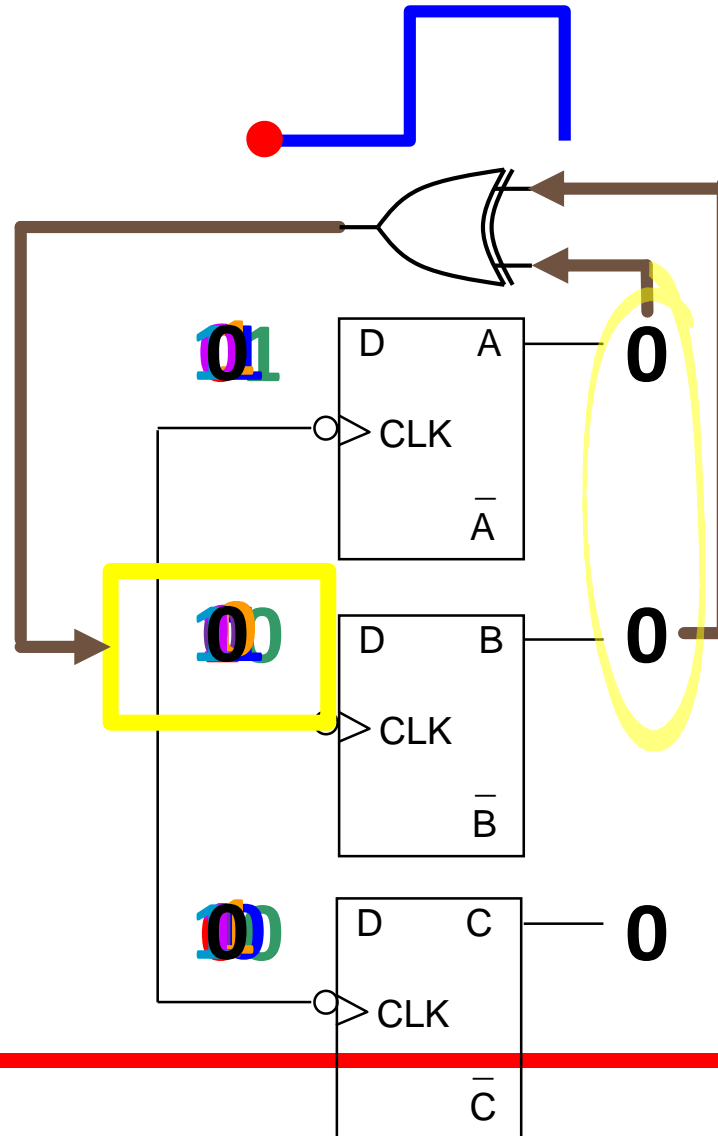



# Counter Animation



# Counter Animation

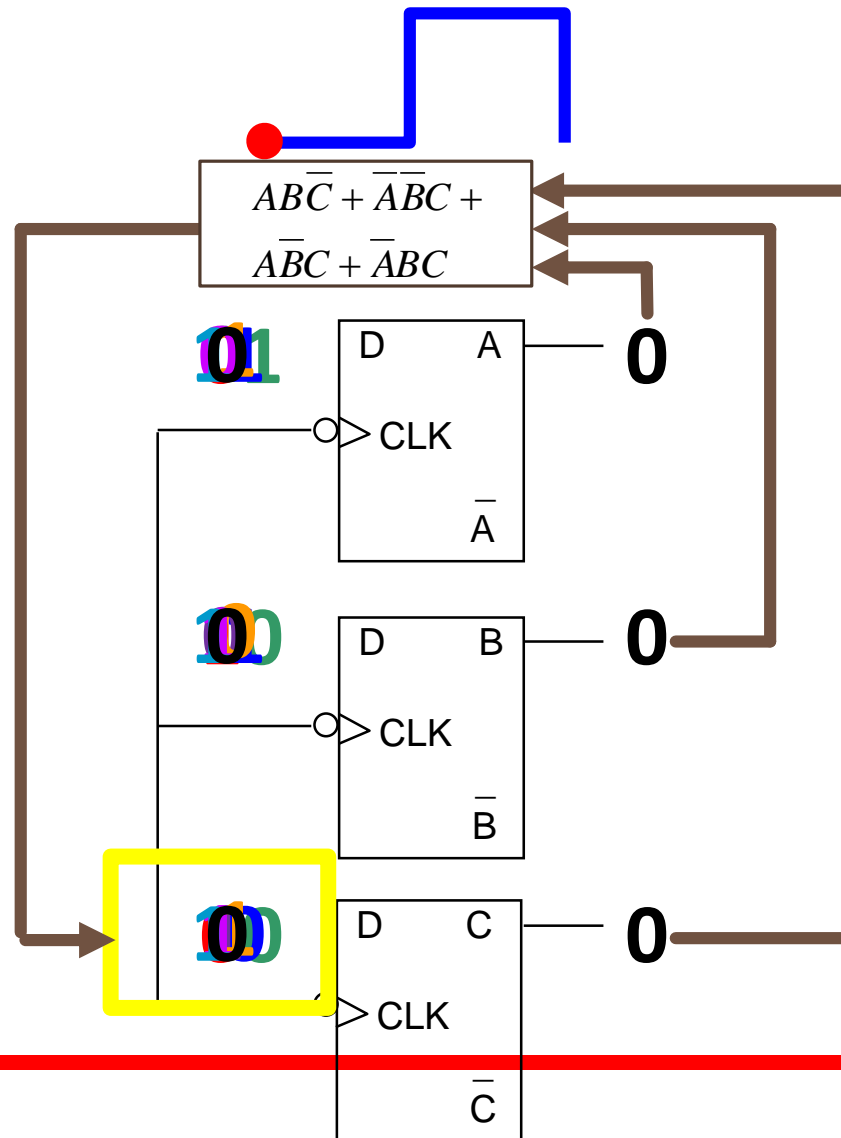


# Counter Animation

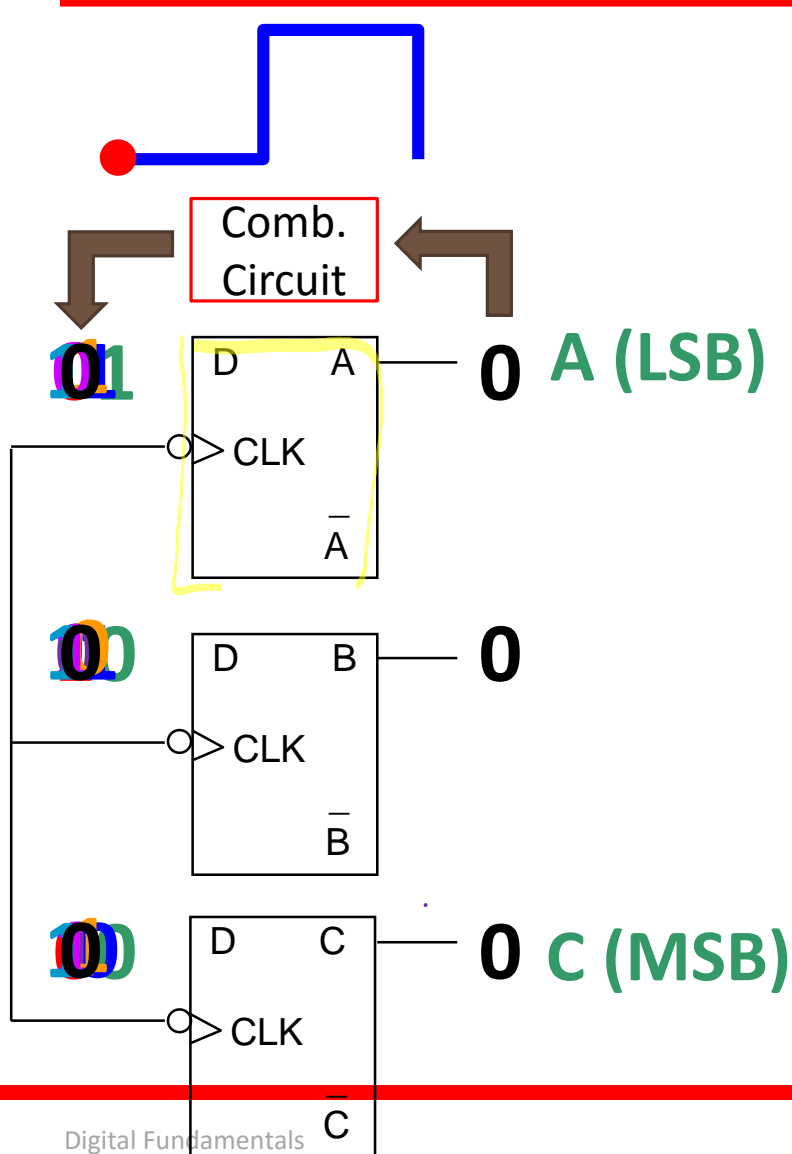 

C	B	A	$C^+$	$B^+$	$A^+$
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	0

# Next State Table

 

Present-state outputs

Next-state outputs

C	B	A	C <sup>+</sup>	B <sup>+</sup>	A <sup>+</sup>
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	0

C, B, A

BA \ C	0	1
00	1	1
01	0	0
11	0	0
10	1	1

$D_A = \bar{A}$

Next-State Table

# Next State Table

Present-state outputs

Next-state outputs

C	B	A	C <sup>+</sup>	B <sup>+</sup>	A <sup>+</sup>
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	0

Next-State Table

BA \ C	0	1
00	0	0
01	1	1
11	0	0
10	1	1

$$D_B = A\bar{B} + \bar{A}B = A \oplus B$$

# Next State Table

Present-state outputs

Next-state outputs

C	B	A	C <sup>+</sup>	B <sup>+</sup>	A <sup>+</sup>
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	0

Next-State Table

BA \ C	0	1
00	0	1
01	0	1
11	1	0
10	0	1

$$D_C = ABC\bar{C} + \bar{B}C + \bar{A}C$$

# Design Method – Cont'd

Step 4

- Realize the circuit.

Present-state outputs      Required FF input

Present-state outputs			Required FF input		
C	B	A	$D_C$	$D_B$	$D_A$
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	0

BA	C	
	0	1
00	0	1
01	0	1
11	1	0
10	0	1

$$D_C = ABC\bar{C} + \bar{B}C + \bar{A}C$$

BA	C	
	0	1
00	0	0
01	1	1
11	0	0
10	1	1


$$D_B = A\bar{B} + \bar{A}B = A \oplus B$$

BA	C	
	0	1
00	1	1
01	0	0
11	0	0
10	1	1

$$D_A = \bar{A}$$



## Synchronous 3-bit counter

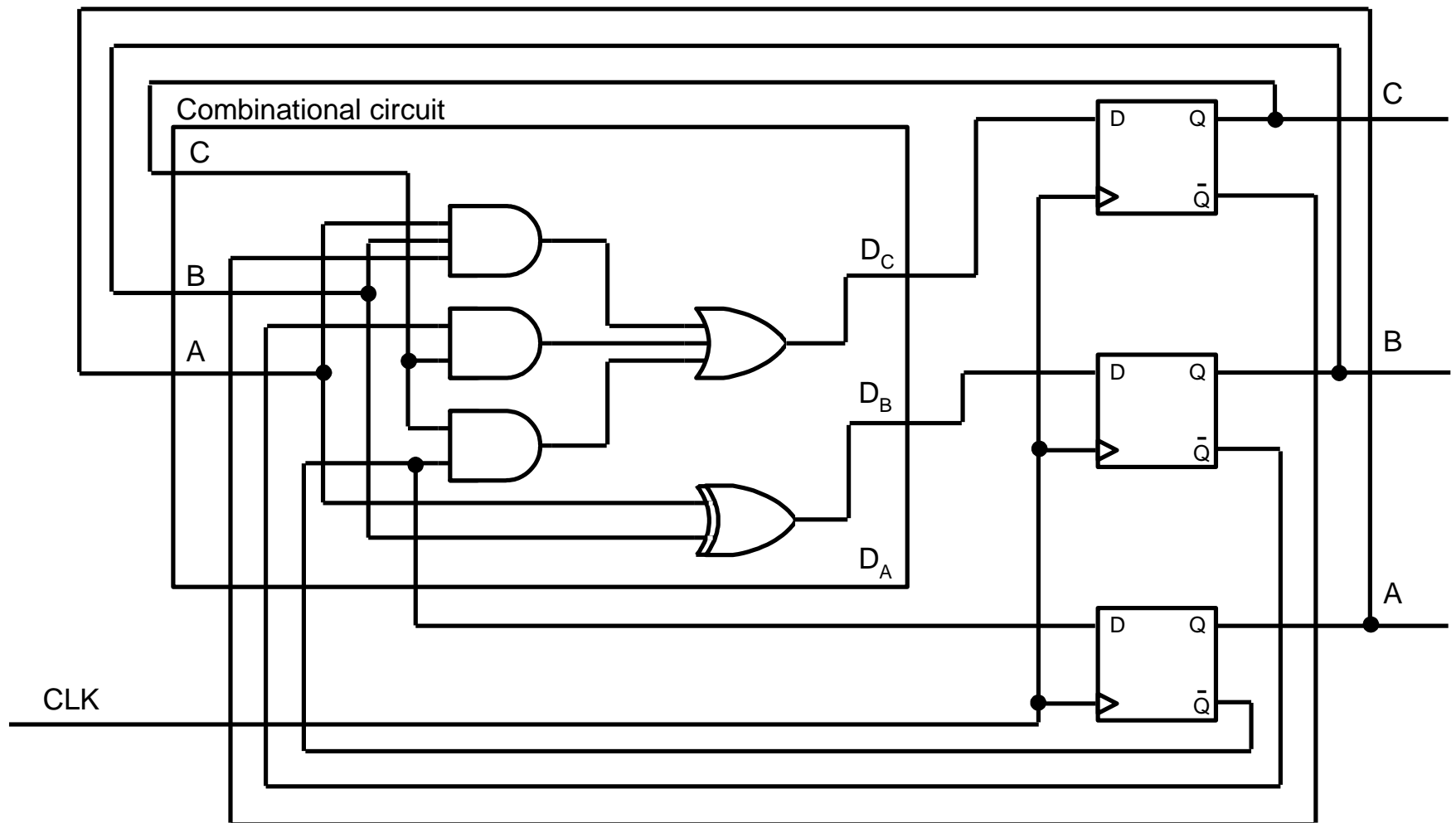

# SEQUENTIAL CIRCUITS - III



---

DESIGN METHOD FOR SYNCHRONOUS COUNTERS


# Design Method - Synchronous Counters

Goal : Given the state diagram of a counter realize it using common FFs (and combinational logic).

  *Example* : Design a **3-bit counter** having the following state diagram. Use **D FFs**.



3-bit synchronous counter

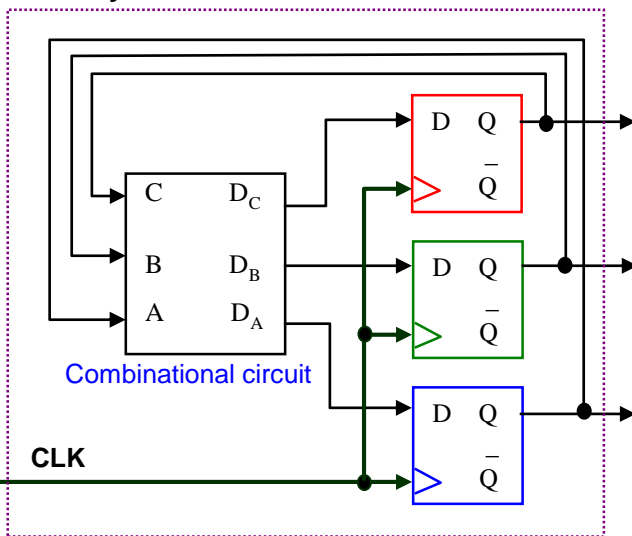

FF outputs are **fed back** to **combinational circuit** inputs.

**Combinational circuit** outputs  $D_A$ ,  $D_B$ , &  $D_C$  are connected to D FF inputs and will **be transferred to the output at next active clock edge**.


**Key:** Design **combinational circuit** to **take previous counter outputs & produce the next state**.

*Systematic design method is similar to that used for FF conversion considered before.*

# Design Method : Steps
 
## Step 1

- Draw a **State Diagram** for the desired **Count Sequence**





## Step 2

- Determine the **Functional Block Diagram** of the **N-bit Counter**.

- 1) Number of flip-flops?
- 2) Inputs and Outputs of combinational circuit?

3-bit synchronous counter

 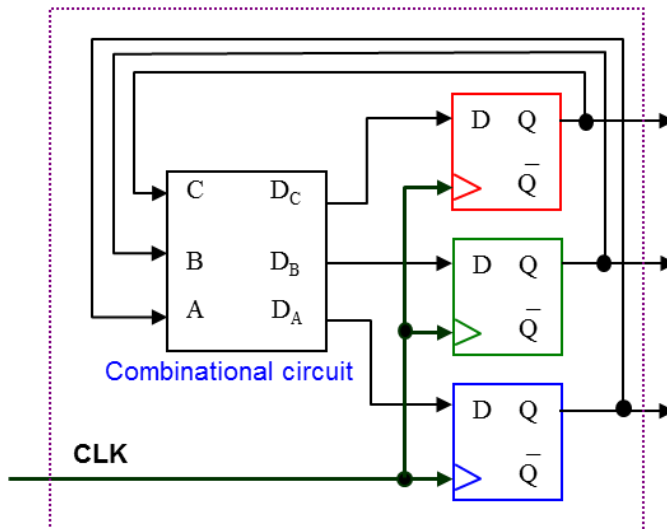

### Combinational Circuit

**Inputs:** Present-state counter outputs ( $A, B, C$ ).

**Outputs:** Next-state counter outputs to connect to FF inputs. ( $D_A, D_B, D_C$ )


# Design Method – Cont'd

## Step 3A

- **Truth table** of the **combinational circuit**.  
A. Determine **next state table** for the counter.

Present-state outputs			Next-state outputs		
C	B	A	C <sup>+</sup>	B <sup>+</sup>	A <sup>+</sup>
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	0

Next-State Table

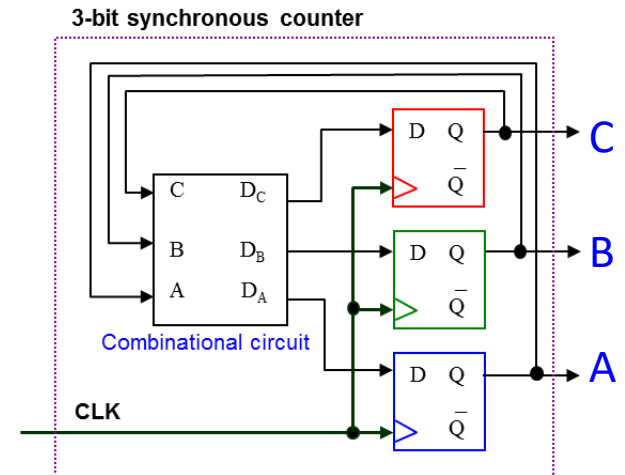

A **synchronous counter** can be realized with **D FFs** or with any other FF

# Design Method – Cont'd


**\*Excitation Table :**  
Specifies what the FF inputs should be for a specific  $Q \rightarrow Q^+$  transition to occur.

## Step 3B

- **Truth table of the combinational circuit.**  
B. Using the **excitation table**, determine the output values of the **combinational circuit**.

Present-state outputs			Next-state outputs			Required FF input		
C	B	A	C <sup>+</sup>	B <sup>+</sup>	A <sup>+</sup>	D <sub>C</sub>	D <sub>B</sub>	D <sub>A</sub>
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	0
0	1	0	0	1	1	0	1	1
0	1	1	1	0	0	1	0	0
1	0	0	1	0	1	1	0	1
1	0	1	1	1	0	1	1	0
1	1	0	1	1	1	1	1	1
1	1	1	0	0	0	0	0	0

Next-State Table

 


D Flip Flop  
Excitation Table

Q	Q <sup>+</sup>	D
0	0	0
0	1	1
1	0	0
1	1	1

$$D \Leftrightarrow Q^+$$

 We now have a truth table for the combinational circuit!



# Design Method – Cont'd

Step 4

- Realize the circuit.

Present-state outputs      Required FF input

C	B	A	$D_C$	$D_B$	$D_A$
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	0

BA \ C	0	1
00	0	1
01	0	1
11	1	0
10	0	1

$$D_C = ABC\bar{C} + \bar{B}C + \bar{A}C$$


BA \ C	0	1
00	0	0
01	1	1
11	0	0
10	1	1

$$D_B = A\bar{B} + \bar{A}B = A \oplus B$$

BA \ C	0	1
00	1	1
01	0	0
11	0	0
10	1	1

$$D_A = \bar{A}$$

## Synchronous 3-bit counter

 



# Synchronous Counter Example 2

---

Design a **synchronous counter** with count sequence using DFFs:


**101**, 001, **000**, **010**, **110**, 100, **101**, ... (mod-6).

The counter also has an external active high synchronous CLEAR input which will clear the counter to **000** at next **active clock edge** when set to '1'.


e.g. **101**, 001, **000**, **010**, **110**, 100, **000**, 010...



# 1) State Diagram

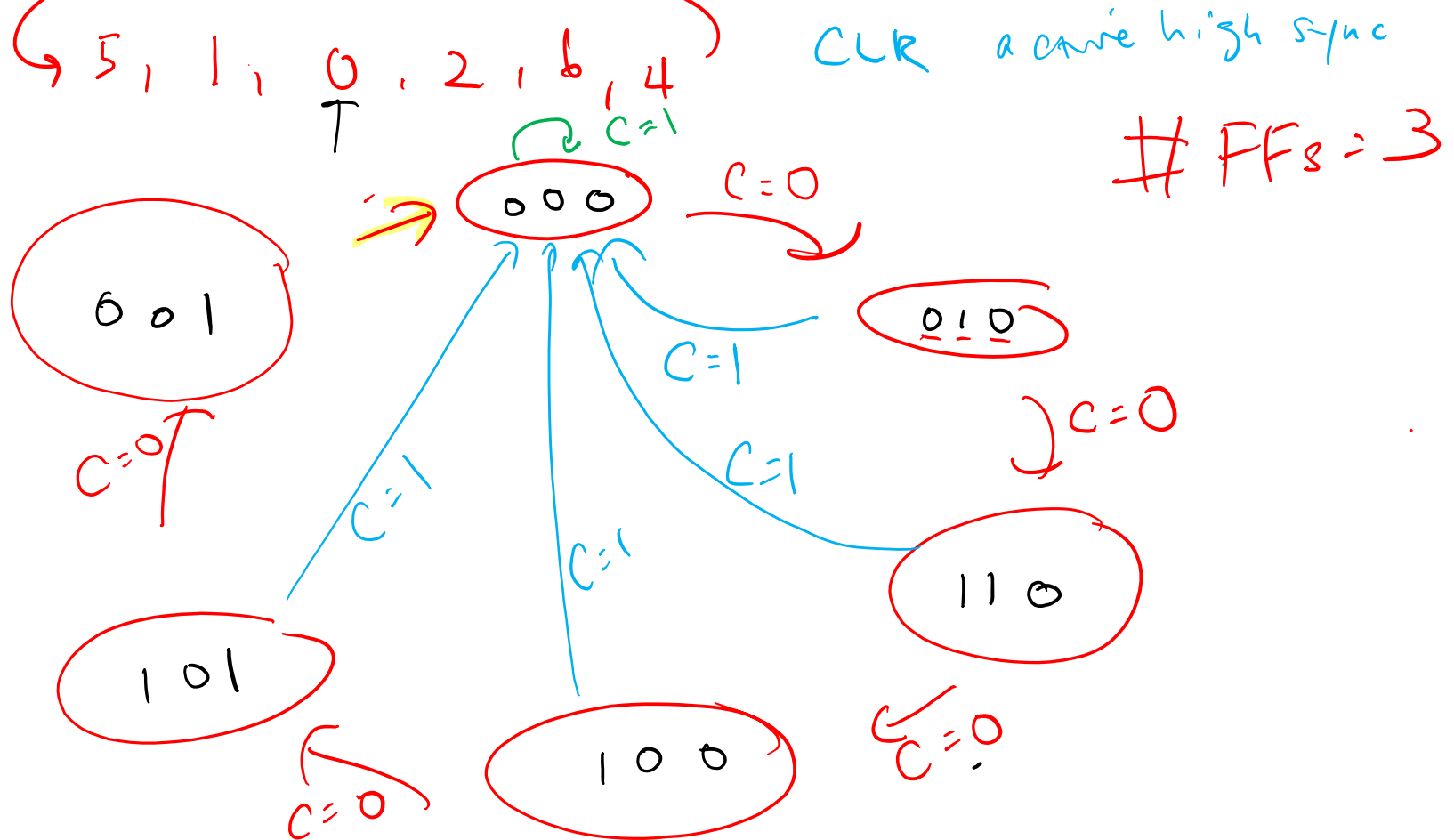

## 2) Functional Block Diagram

 

### 3) Next State Table / Truth table of C.C.

CLR	C	B	A	$D_C/C^+$	$D_B/B^+$	$D_A/A^+$
1	X	X	X	0	0	0
0	1	0	1	0	0	1
0	0	0	1	0	1	0
0	0	0	0	0	1	0
			...			




# 4) Final Implementation

---

**Step1:** Write state diagram.

**Step2:** Determine functional block diagram of counter.

 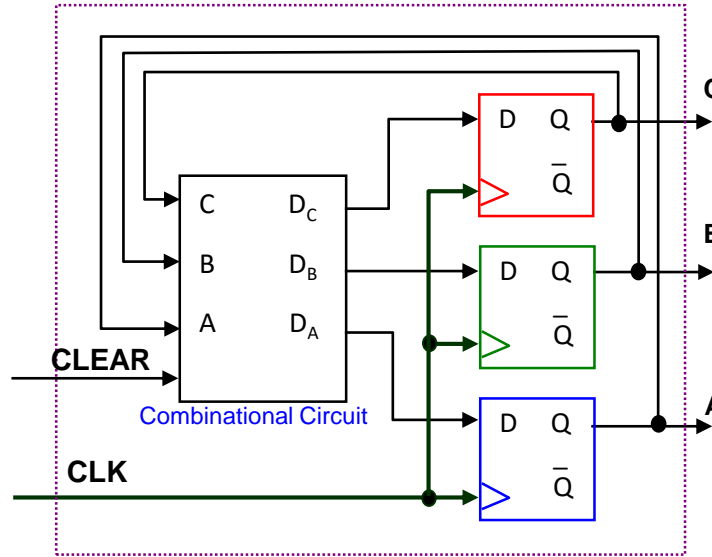 **Step3 :** Functional block diagram of combinational circuit.



**Step4 :** Get TT of combinational circuit using FF excitation table.

**Step5 :** Realize circuit.

CLEAR	C	B	A	C <sup>+</sup>	B <sup>+</sup>	A <sup>+</sup>	D <sub>C</sub>	D <sub>B</sub>	D <sub>A</sub>
0	0	0	0	0	1	0	0	1	0
0	0	0	1	0	0	0	0	0	0
0	0	1	0	1	1	0	1	1	0
0	0	1	1	X	X	X	X	X	X
0	1	0	0	1	0	1	1	0	1
0	1	0	1	0	0	1	0	0	1
0	1	1	0	1	0	0	1	0	0
0	1	1	1	X	X	X	X	X	X
1	X	X	X	0	0	0	0	0	0

SOP for flip-flop inputs

$$D_C = \overline{CLEAR} \cdot B + \overline{CLEAR} \cdot C \cdot \bar{A}$$

$$D_B = \overline{CLEAR} \cdot \bar{C} \cdot \bar{A}$$

$$D_A = \overline{CLEAR} \cdot C \cdot \bar{B}$$