

EE2026

Digital Design

Chua Dingjuan
elechuad@nus.edu.sg

Module Outline

◦ Part 1

- Number systems
- Boolean Algebra and logic gates
- Gate-level design and minimization
- Combinational logic circuits and design
- Logic IC family

◦ Part 2

- Sequential logic circuits
 - Flip-Flops, Counters, (Shift Registers)
- Verilog review
- Verilog behavioral and structural modeling
- Digital finite state machine design
- Modeling of FSMs using Verilog

Expected Learning Outcomes

- Able to design basic sequential logic circuits using flip-flops.
- Able to design, build and test digital systems using FPGAs.
- Able to design, model and simulate digital logic circuits using Verilog.
- Able to design and model simple state machines based on the FSM approach.

EE2026 Tutorial & Lab Schedule


Week	Tutorials	Lab	Quiz
WK 6	--	Lab 3 – Sequential Circuits 1	
Recess Week			
WK7	Tutorial – 6	Lab 4 – Sequential 2	
WK8	Tutorial – 7	Project Lab 1	
WK9	Tutorial – 8	Project Lab 2	
WK10	Tutorial – 9	Project Lab 3	
WK11	Tutorial – 10		
WK12		Project Lab 4 / Project Evaluation	
WK13			Final Quiz

SEQUENTIAL CIRCUITS - I





©COPYRIGHT CHUA DINGJUAN. ALL RIGHTS RESERVED.

Design a circuit to do this >>

 

When the button is pushed :

  - 1) Turn On the light *if* it is Off
- 2) Turn Off the light *if* it is On




What is missing?

- 1) Remembering the previous state of the bulb → *MEMORY*
- 2) Responding to an input *EVENT* (cf. input value)

Sequential Logic Circuits?

Combinational Logic Circuits:

- Outputs depend on current inputs

 


Sequential Logic Circuits:

- Outputs depend on **current and previous** inputs → Memory!
- Requires separation of previous, current, future : states
- 2 Types of sequential circuits:

Synchronous	Asynchronous
Clocked: need a clock input	Unclocked
Responds to inputs at discrete time instants governed by a clock input	Responds whenever input signals change


SR Flip-flop (FF)

 

The simplest memory element has two stable states :

Flip-Flop (FF) → it can store 1 bit of information

 Most basic FF : **Set-Reset** (SR) Flip-flop / Latch




S	R	Output	Q+
0	0		
0	1		
1	0		
1	1		
0 0 is the rest state			

Implemented with NOR / NAND gates



SR Flip-flop (FF)

 


 
NOR Implementation

S	R	Output Q
0	0	
0	1	
1	0	
1	1	

A	B	NOR

SR Flip-flop (FF)

- FF can **record** and **store** transient events. 
- Switching is not instantaneous → **propagation delays**




S	R	Output
0	0	Hold
0	1	$Q = 0$
1	0	$Q = 1$
1	1	Invalid
0 0 is the rest state		

1) Assume that the *rest state* is:






$S = R = 0$; let $Q = 0$, $\bar{Q} = 1$

2) If $S \rightarrow \text{pulse}$ while $R = 0 \Rightarrow Q = 1$, $\bar{Q} = 0$, i.e., the event (S going high) is recorded and stored as $Q = 1$.

$R = 0$

 

A Simple Application...

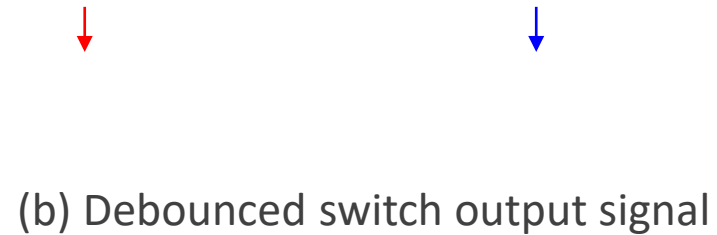    


- Mechanical switches bounce before settling down which may cause problems as inputs.
- Switch **debouncing** is a common use of S-R FFs.

S	R	Output
0	0	Hold
0	1	Q = 0
1	0	Q = 1
1	1	Invalid
0 0 is the rest state		

JK FF

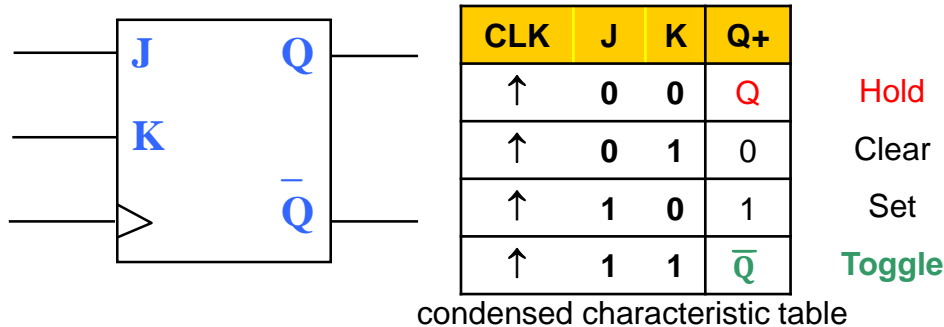The JK FF is based on SR with 2 improvements : _____ & _____




CLK	J	K	Q	Q+
↑	0	0	0	0
↑	0	0	1	1
↑	0	1	0	0
↑	0	1	1	0
↑	1	0	0	1
↑	1	0	1	1
↑	1	1	0	1
↑	1	1	1	0

characteristic table


The JK FF is a **synchronous** circuit:

 - **Clock input** is a controlling input.
It specifies when circuit read inputs / change outputs.
- **Synchronous circuits** respond only at the _____ clock edges
i.e., **LOW** → **HIGH**, **HIGH** → **LOW** transitions




- At any other time, changing inputs have no effect on the output.

Respond @ Active Clock Edges

 

- When inputs don't change → FF outputs don't change.
- If inputs change → FF output changes state only at active clock edge.

FF Timing Parameters

 

- t_{setup} : minimum time before the *active* clock edge by which FF inputs must be stable.
- t_{hold} : minimum time inputs must be stable after *active* clock edge
- t_{pHL} : time taken for FF output to change state from High to Low.
- t_{pLH} : time taken for FF output to change state from Low to High.



What happens if inputs change state right at the *active* clock transition?

Answer: output is _____

Thus, input changes must meet required *setup* & *hold* times of device
== Operating Speed of device


<http://www.ti.com/product/SN74LS107A>

Commercially Available JK FFs

  

74'107 with asynchronous clear


CLK	CLR	J	K	Q ⁺
X	L	X	X	L
↓	H	L	L	Q
↓	H	L	H	L
↓	H	H	L	H
↓	H	H	H	\bar{Q}

 


74'109 with direct set & direct clear

CLK	PR	CLR	J	K	Q ⁺
X	L	H	X	X	H
X	H	L	X	X	L
X	L	L	X	X	not allowed
↓	H	H	L	L	Q
↓	H	H	L	H	L
↓	H	H	H	L	H
↓	H	H	H	H	\bar{Q}


Other Flip-Flops...

 


CLK	D	Q ⁺
↑	0	0
↑	1	1

 

EN	D	Q ⁺
0	X	No change
1	0	0
1	1	1

 


CLK	T	Q ⁺
↑	0	Q
↑	1	\bar{Q}

 


CLK	J	K	Q ⁺
↑	0	0	Q
↑	0	1	0
↑	1	0	1
↑	1	1	\bar{Q}

Since **T Flip-flops** are easy to construct from other FFs, they are not available commercially.


Verilog Time! – D-FF

 

CLK	D	Q+
↑	0	0
↑	1	1

 

Verilog Time! – D-FF

 

CLK	D	Q+
↑	0	0
↑	1	1



↑ always @ (posedge __)

↓ always @ (negedge __)

```
module dff ( input  
            output  
            );
```

```
always @ (posedge clock)
```

```
begin
```

```
end
```

```
endmodule
```

Some notes on: `always` & `reg`

Registers

- Anything assigned in an `always` block *must* be type `reg`
- In Verilog, the term register (`reg`) simply means a variable that can hold a value
- Values of registers can be changed instantaneously. This is different from the `wire` type!

Always Block

- Conceptually, the `always` block runs *once* when a signal in *sensitivity list* changes value.
- Statements within `always` block are executed *sequentially*.
- `begin` and `end` behave like parentheses/brackets
- No ~~`assign`~~!

Summary

- SR Flip Flop & Applications
- JK Flip Flop
- FF Timing Parameters
- Commercial JK Flip Flops
- Verilog description of D Flip Flop

Practice Question

Given the circuit diagram below, complete the timing diagram below by filling in Q and \bar{Q} . Assume that the initial value of Q is '0' and include all propagation delays.

